
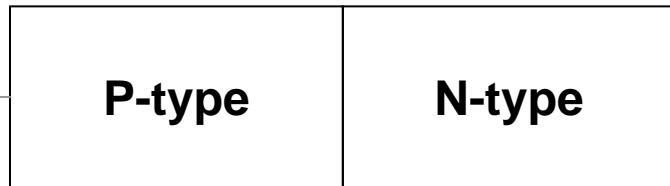


Diode Reverse Recovery and its Effect on Switching Losses

Peter Haaf, Senior Field Applications Engineer
Jon Harper, Market Development Manager
November 2006

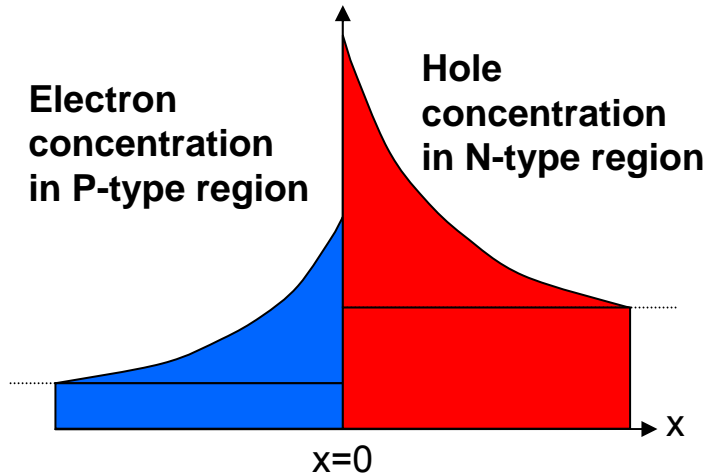
1. Basics
2. Mathematical Estimations
3. Comparison of the Estimations with real measurements
4. Switching Losses vs. Voltage
5. Switching Losses vs. Current
6. E_{ON} Losses during Hard Switching with different Diode Technologies
7. Effect of parallel Caps on Switching Losses
8. Switching Losses vs. rise and fall time
9. Summary

Minority carrier concentration near the junction




Diode conducting

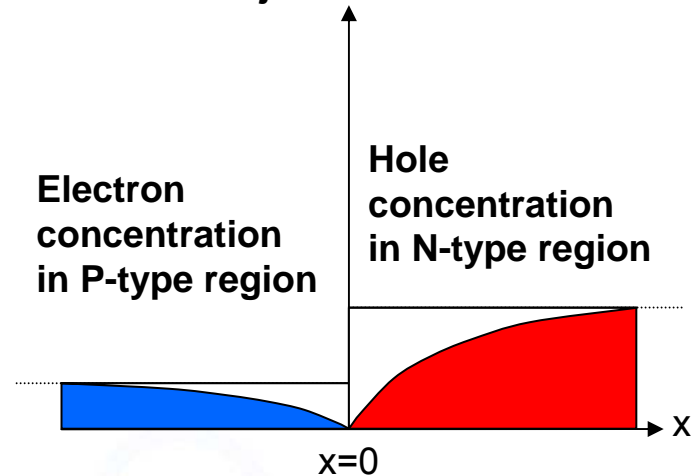Minority carrier concentration near the junction



Diode blocking

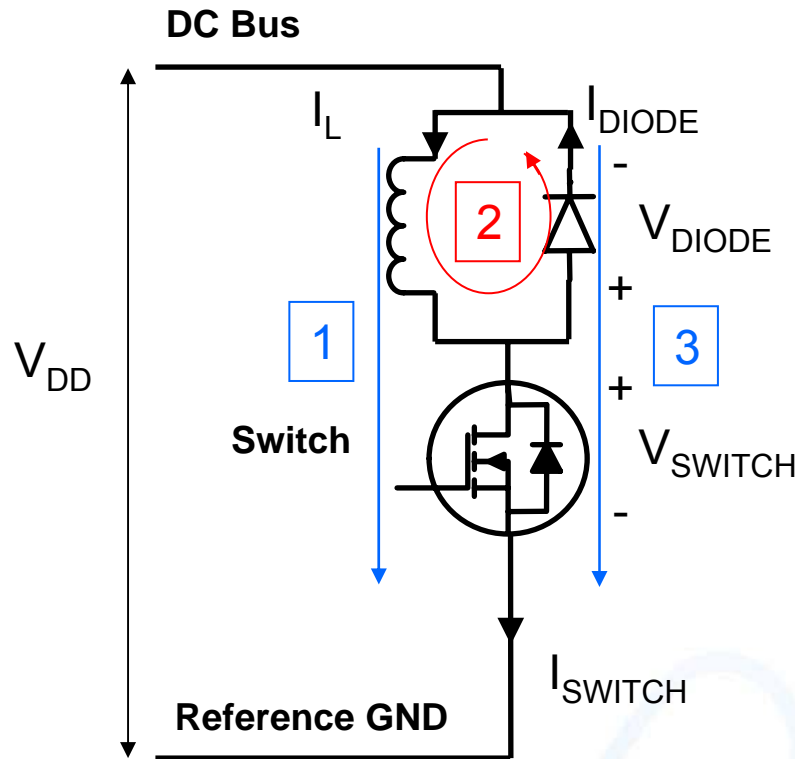

- Step 1: Switch is turned on
Current rises
- Step 2: Switch is turned off
Current is circulating
- Step 3: Switch is turned on
again, Diode is
recovering and
current continues
rising

- Definition of Power Losses

$$P = 1/T * \int V(t) * I(t) dt$$

$$= \text{mean } (V(t) * I(t))$$


$$E = P * t$$

$$= \int V(t) * I(t) dt$$


$$= \text{area } (V(t) * I(t))$$


$$P_{on} = E_{ON} * f;$$

$$P_{off} = E_{OFF} * f$$

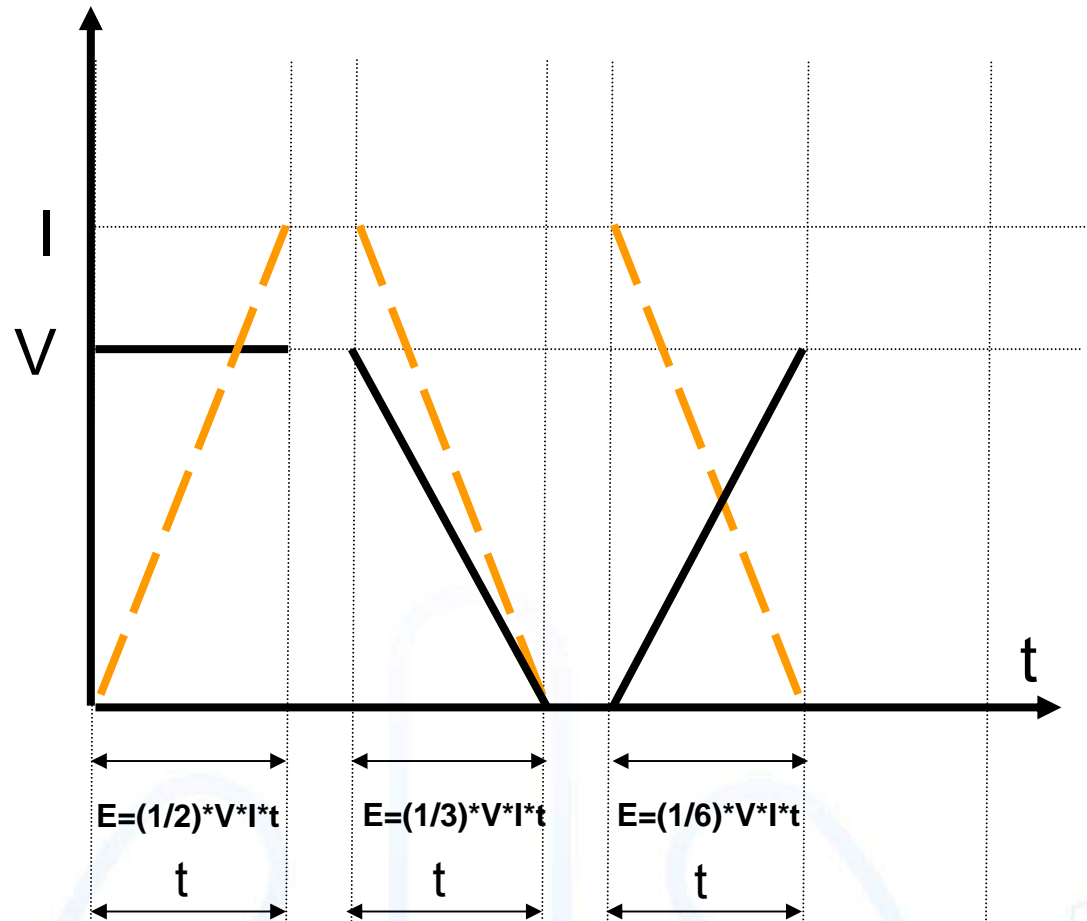


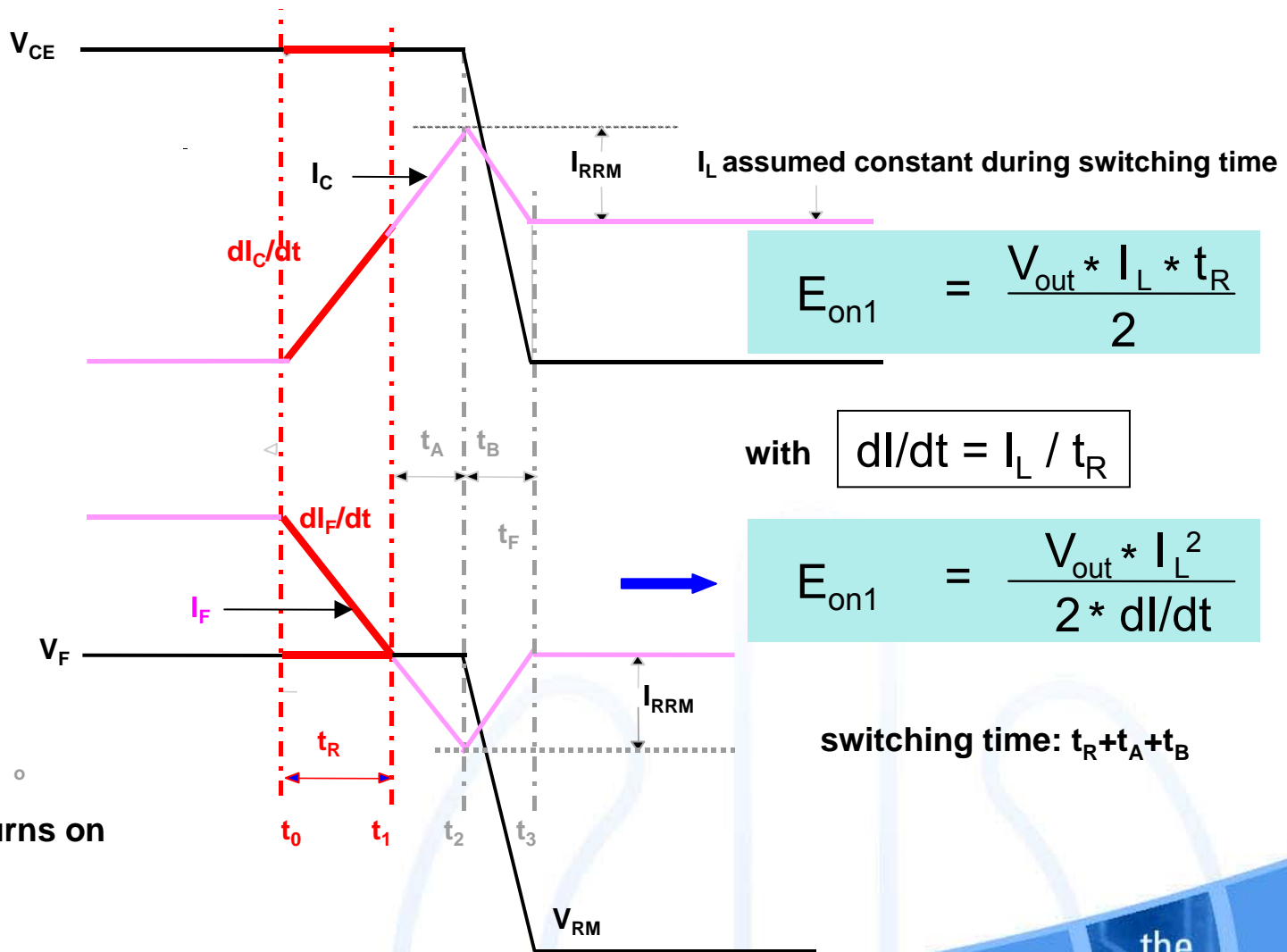Turn On Loss Due to Diode Recovery (Phase t_R)




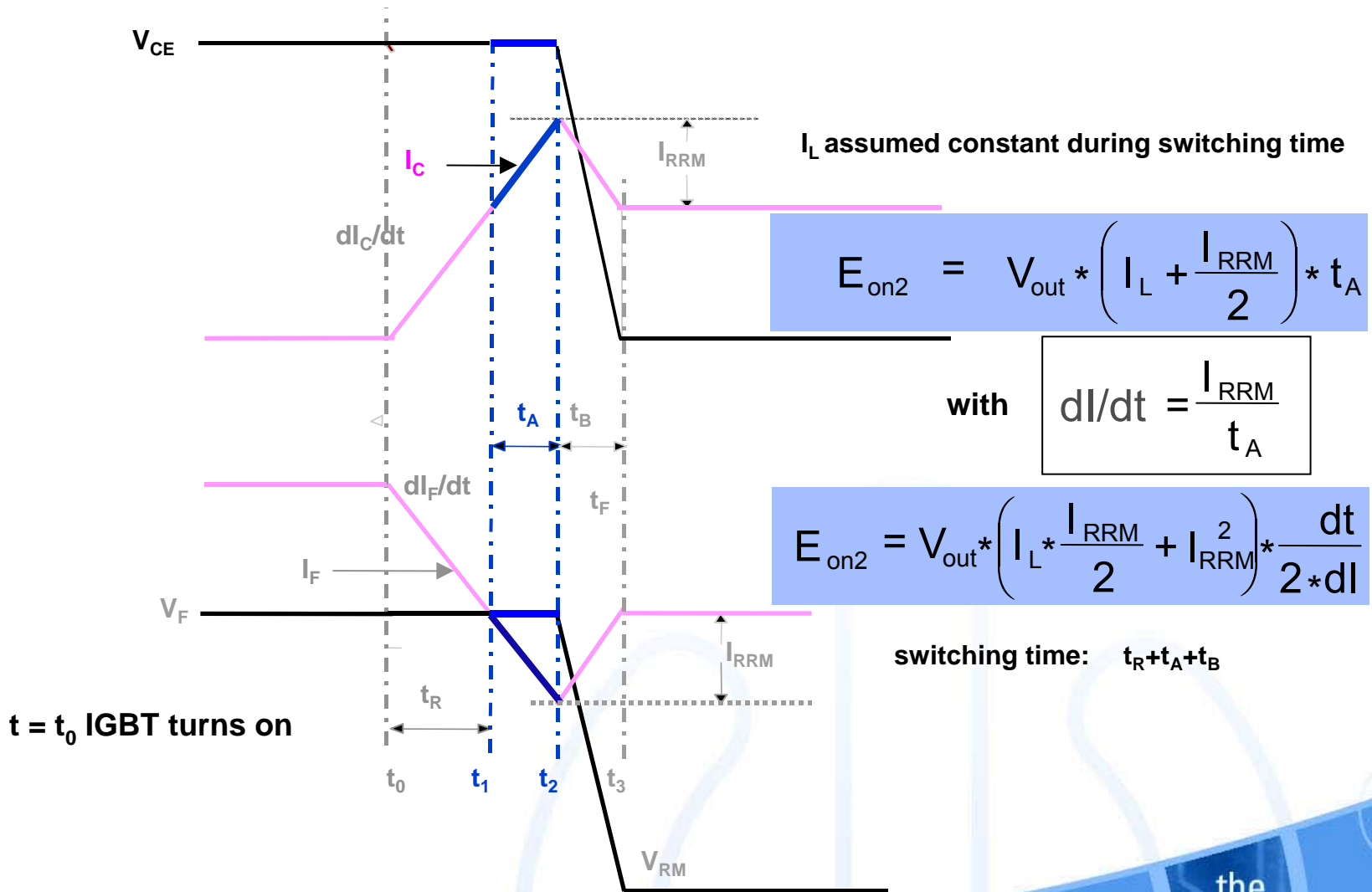

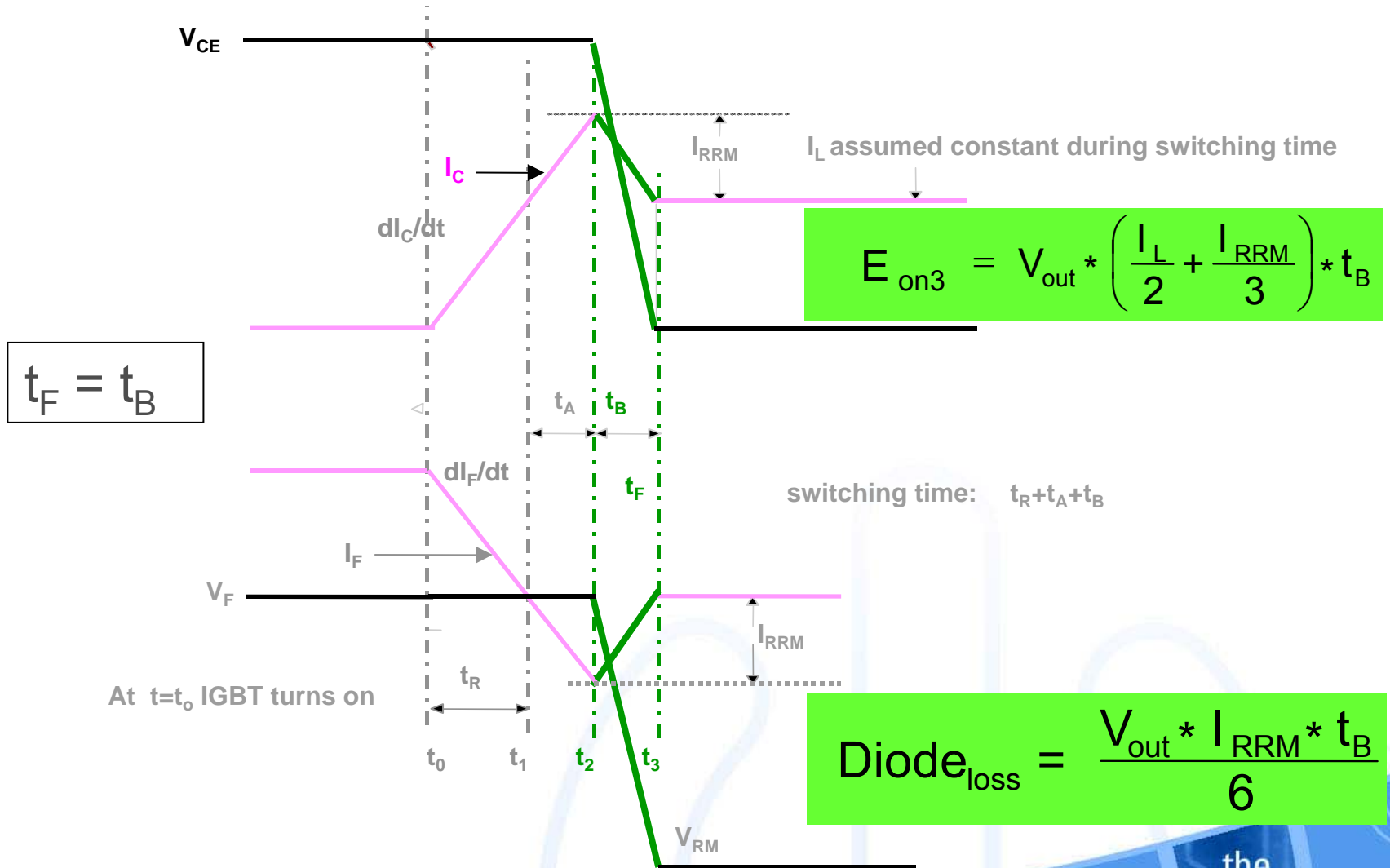Turn On Loss Due to Diode Recovery (Phase t_B)



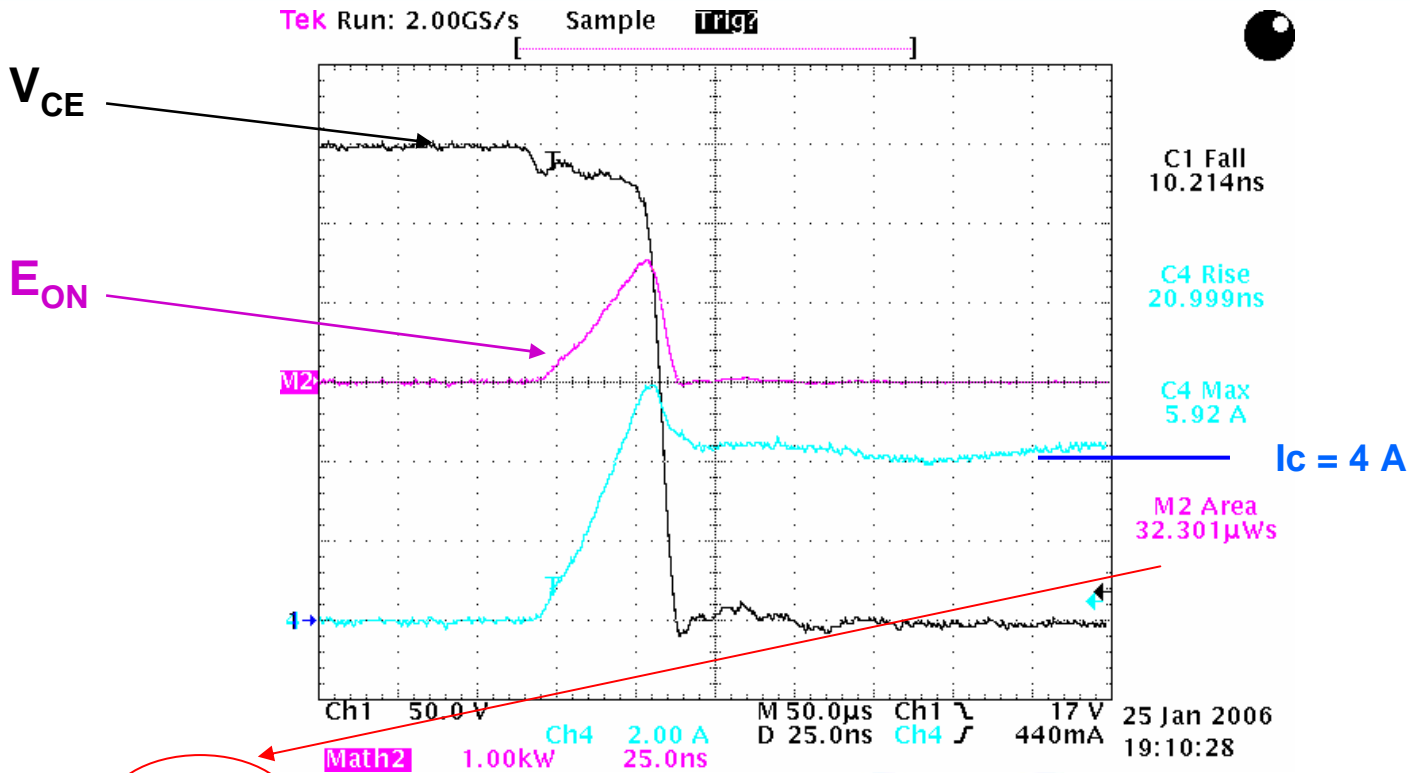Double check of the formulas: Eon calculation vs. measurement



Eon =	32.67 µJ	Pon =	1.63 W	50 (kHz)	Frequency
Eon1 =	11.20 µJ	Pon =	0.56 W	4 (A)	Current
Eon2 =	14.00 µJ	Pon =	0.70 W	280.00 (V)	Udc
Eon3 =	7.47 µJ	Pon =	0.37 W	2.00E+08 (A/s)	dl/dt
Diode:				2 (A)	Irr; Diode
Eoff =	9.33E-01 µJ	Poff =	0.05 W	1.00E-08 (s)	tf fall time

Loss calculation 25 °C and 125 °C

Specification	FFP08S60S		ISL9R860P2	
	T _C =25°C	T _C =125°C	T _C =25°C	T _C =125°C
t _A / ns (typ)	11.9	25.2	16.4	15.1
t _B / ns (typ)	7.1	32.8	60.6	37.9
I _{RRM} / A (typ)	2.2	4.3	3.4	6.5
Q _{RR} / nC (typ)	21	125	150	190
Switch losses example calculation / μJ	118	232	246	220
V _F / V (typical)	2.1	1.6	2.0	1.6

Measured with di/dt=200A/us, see datasheets for full details
 Example: Loss in switch for 8A, di/dt=200A/us, V_{DD}=390V
 Equations in Power Seminar 2007 documentation



Loss calculation 75 °C and 100 °C

Specification	FFP08S60S		ISL9R860P2	
	T _C =75°C	T _C =100°C	T _C =75°C	T _C =100°C
t _A / ns (typ)	18.5	21.9	15.8	15.5
t _B / ns (typ)	20	26.4	49.2	43,5
I _{RRM} / A (typ)	3.3	3.8	5.0	5.7
Switch losses example calculation / μJ	172	201	235	228
V _F / V (typical)	1.85	1.725	1.8	1.7
Switching loss @ 100 kHz / W	17.2	20.1	23.5	22.8

Calculated with di/dt=200A/us, see datasheets for full details
 Example: Loss in switch for 8A, di/dt=200A/us, V_{DD}=390V
 Equations in Power Seminar 2007 documentation
 Linear approximation: of ta, tb, Irrm and Vf

6.3 W difference on switching losses


Loss measurements

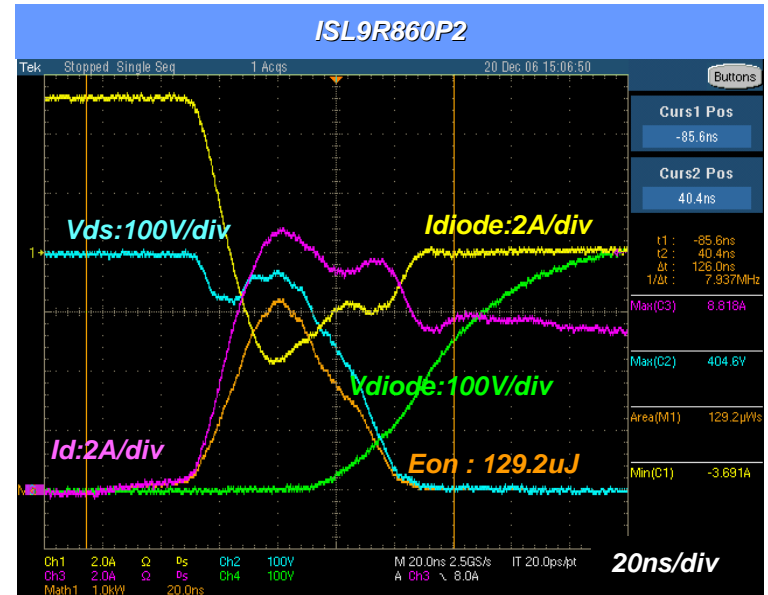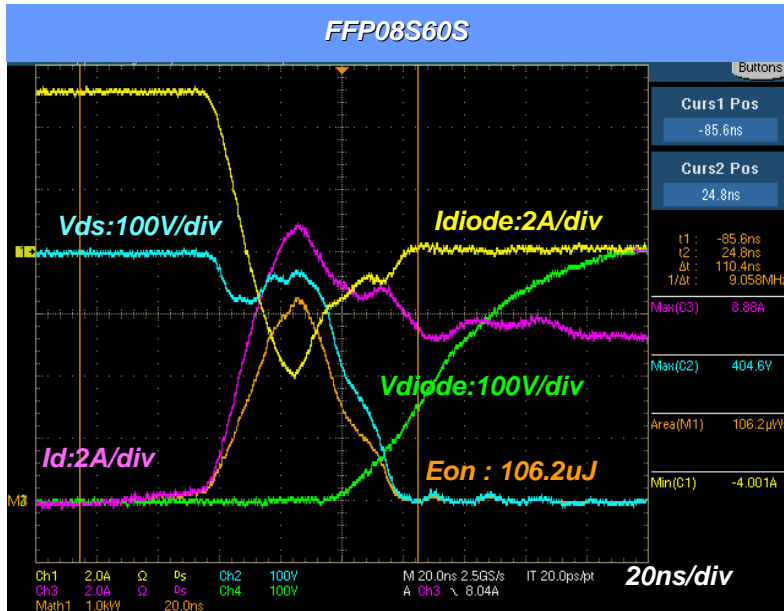


DUTs	Ta	TMOSFET	Tdiode	dTMOSFET	dTdiode	Pin	Vout	Iout	Pout	Efficiency	PF
ISL9R860P2	26.2	120.2	76.7	94.0	50.5	431.2	401.240	0.984	394.70	91.54	0.999
FFP08S60S	26.2	113.3	70.1	87.1	43.9	426.0	401.240	0.984	394.70	92.65	0.999

Test condition : Vin=220Vac, Pout=400W/1A(400W), Fs=100kHz

5.2 W difference in input power

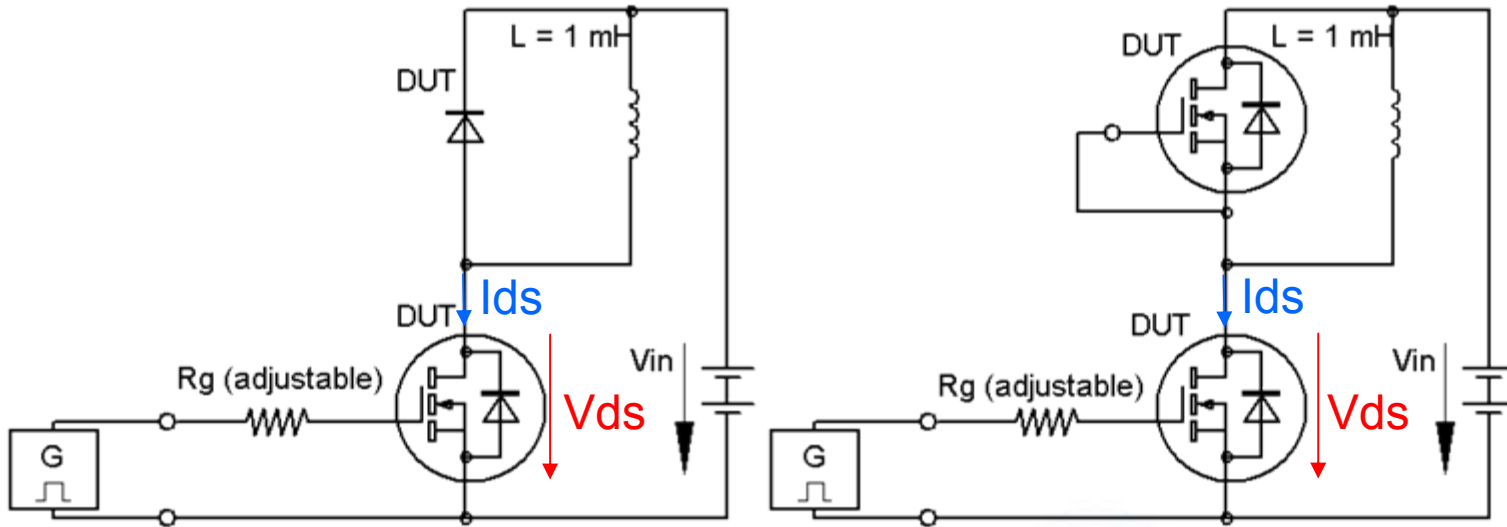


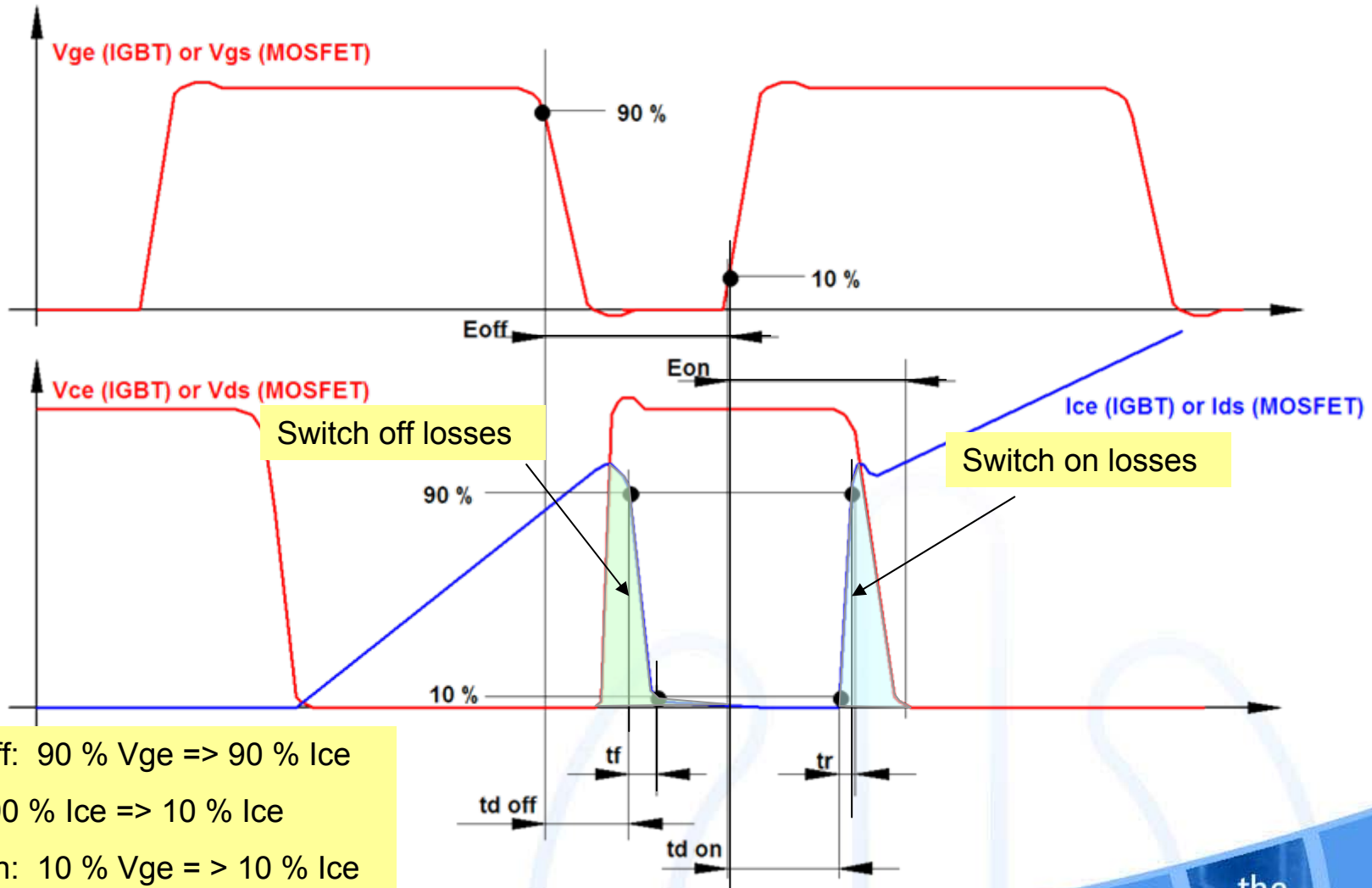Test Circuits which are used for the following measurements



$t_{d\ off}$: 90 % V_{ge} => 90 % I_{ce}
 t_f : 90 % I_{ce} => 10 % I_{ce}
 $t_{d\ on}$: 10 % V_{ge} => 10 % I_{ce}
 t_r : 10 % I_{ce} => 90 % I_{ce}

E_{ON}

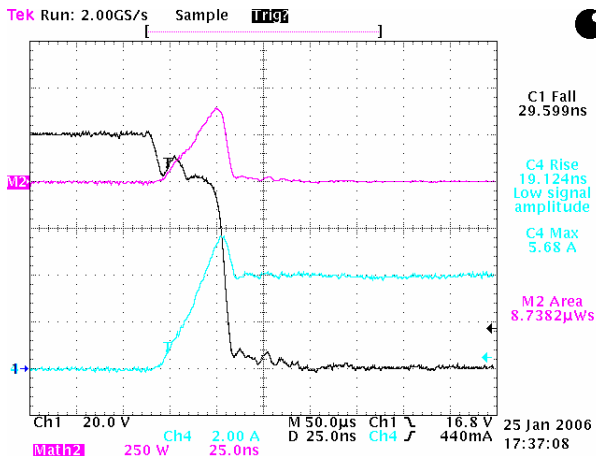



E_{ON} / E_{OFF}
losses

$$V_{IN} = 100V$$

$$E_{ON} = 8.7\mu J$$

$$E_{OFF} = 9.5\mu J$$


E_{OFF}

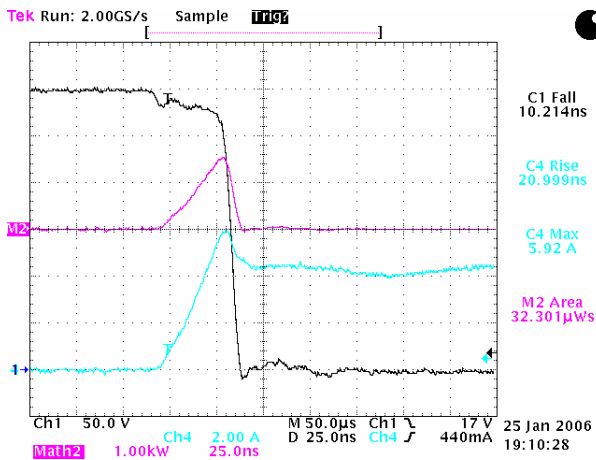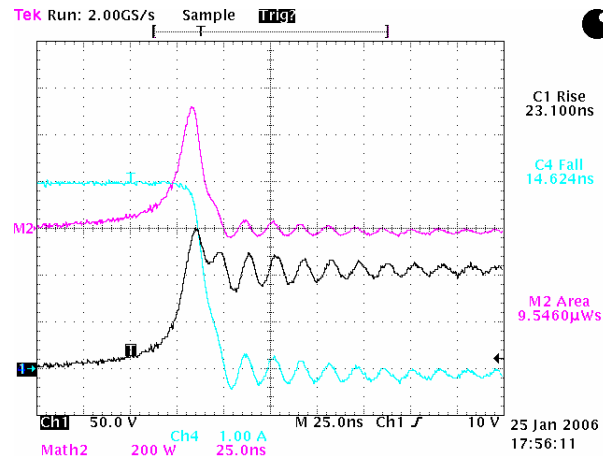


$$V_{IN} = 300V$$

$$E_{ON} = 32.3\mu J$$

$$E_{OFF} = 23.1\mu J$$

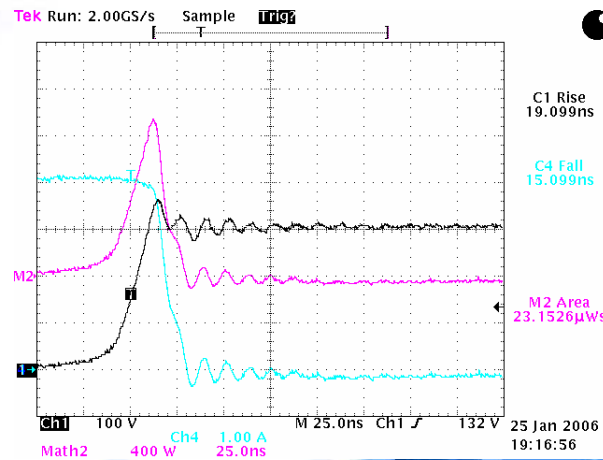


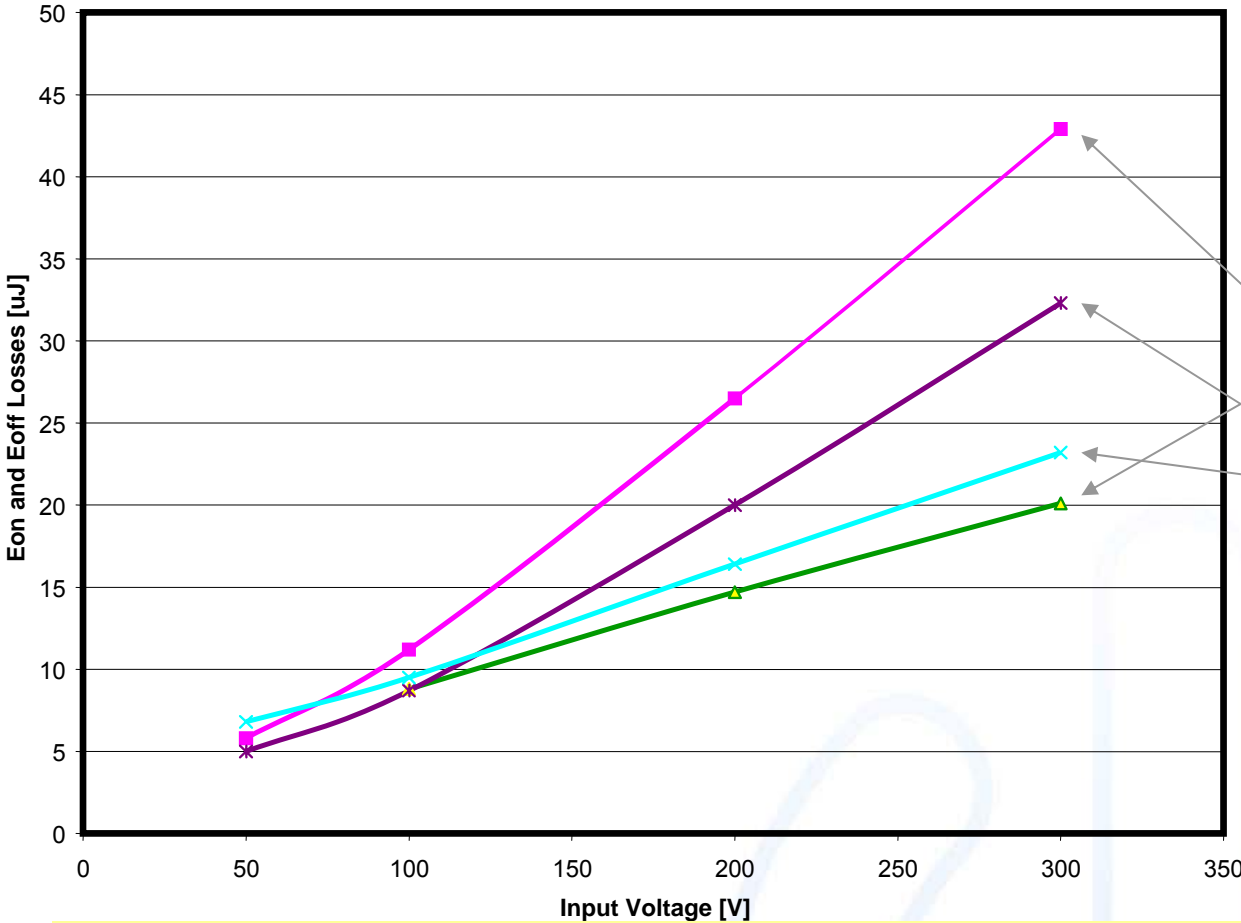Eon and Eoff losses of the FET - FQP9N50C vs. Input Voltage



Comparison of two Stealth™ diodes, which are optimized for hard switching

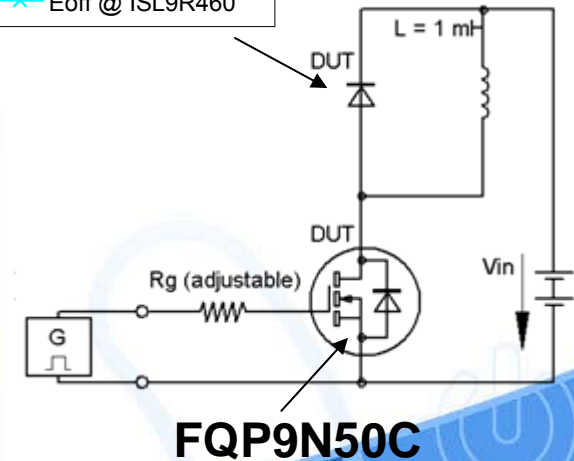
- Eon @ ISL9R1560
- ▲ Eoff @ ISL9R1560
- ✱ Eon @ ISL9R460
- ✕ Eoff @ ISL9R460




Higher Current rating of the Diode will increase Eon, but decrease Eoff (Diode capacitance acts as a snubber). **Eon is dominating!**

Switching Losses vs. Current


FQP9N50C + ISL9R460 @ $V_{IN} = 300V$

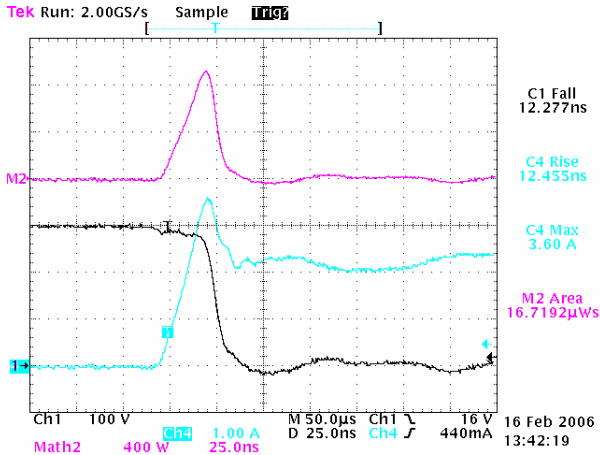


$I = 2A, E_{ON} = 16.7\mu J$

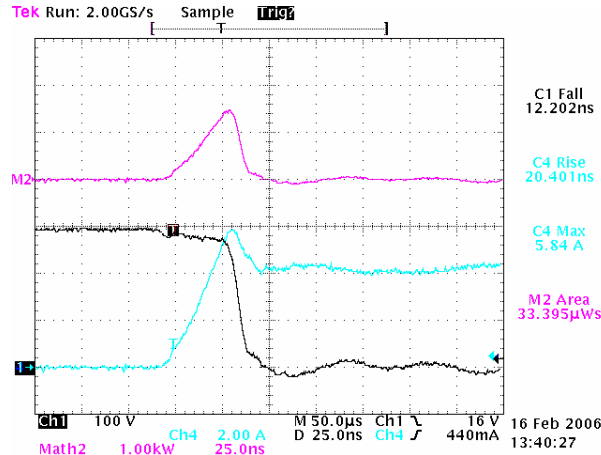


$I = 4A, E_{ON} = 33.4\mu J$

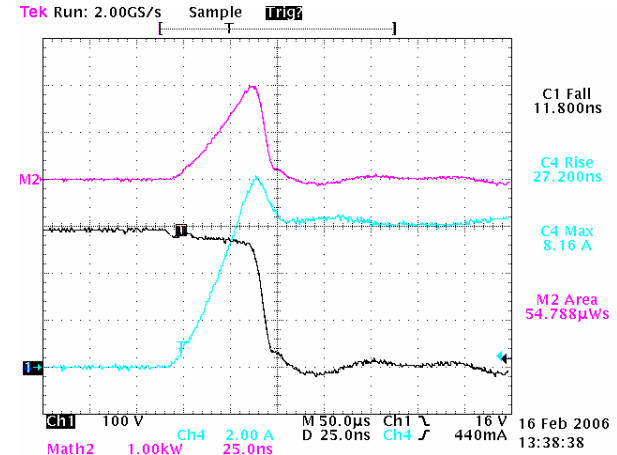


$I = 6A, E_{ON} = 54.8\mu J$

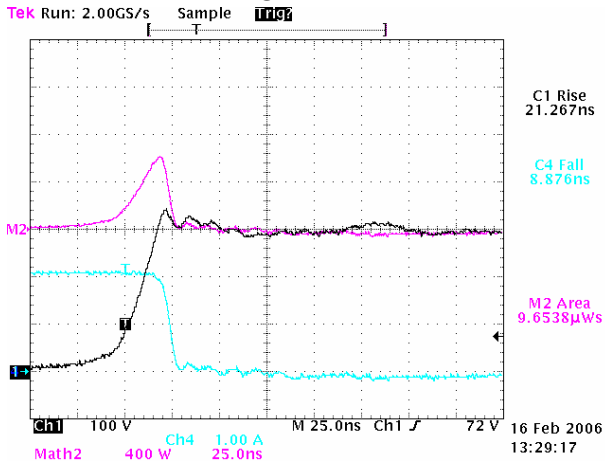

$I = 2A, E_{OFF} = 9.7\mu J$

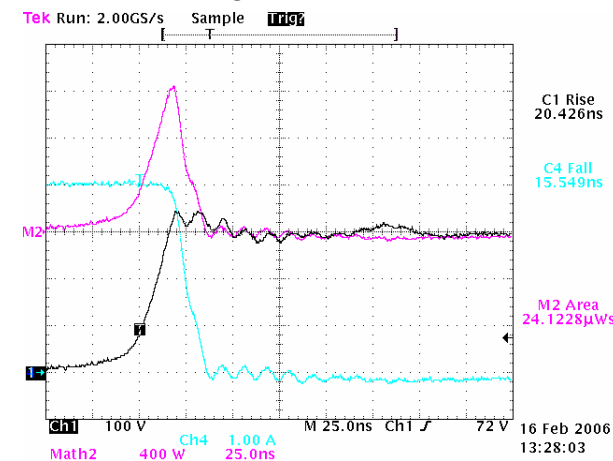




$I = 4A, E_{OFF} = 24.1\mu J$

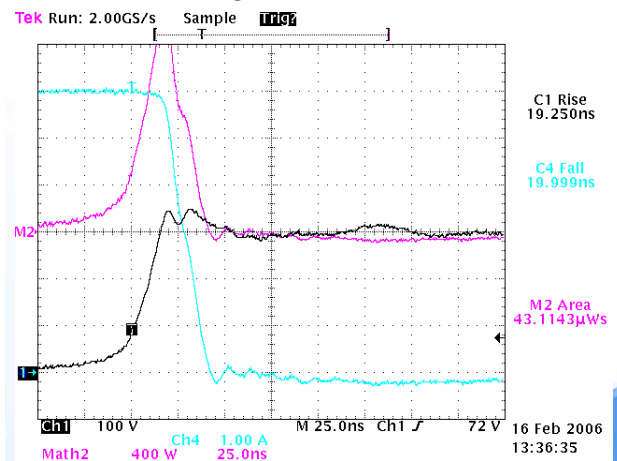

$I = 6A, E_{OFF} = 43.1\mu J$

(nearly) Linear relation between current and losses.

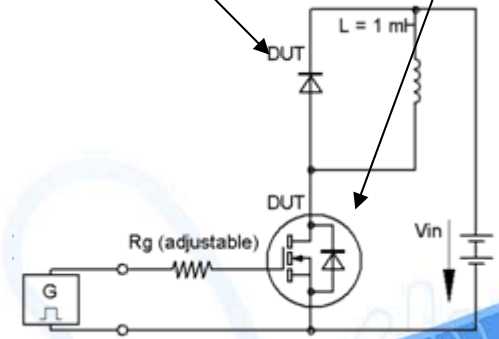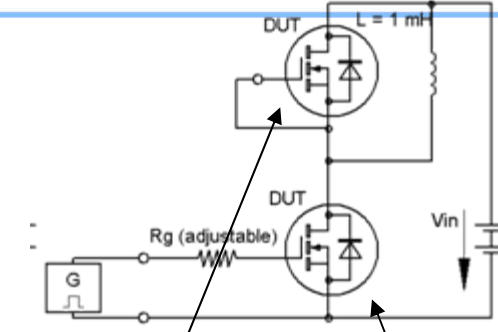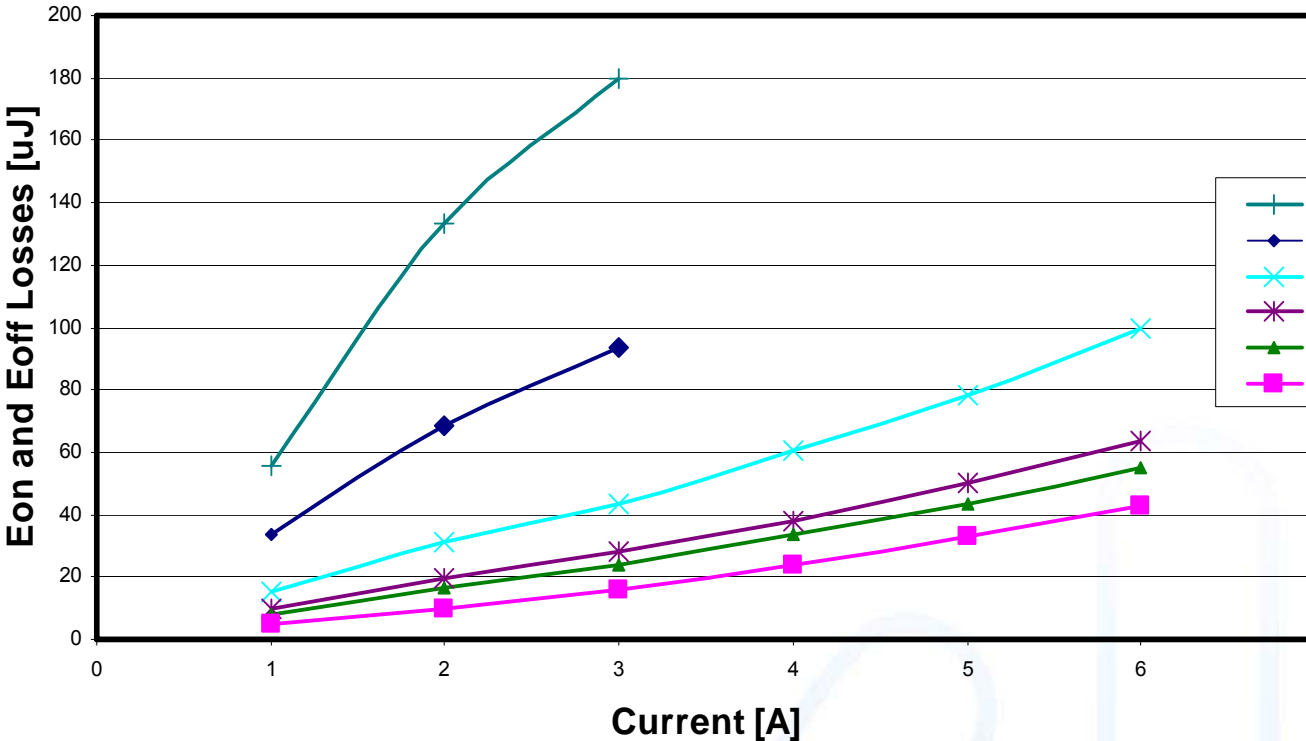Eon and Eoff losses of the FET - FQP9N50C vs. Current





FQP9N50C

Technologies as well as rating will have a big impact on the Eon losses. Fast recovery FETs will lead to significant higher Eon losses compared to single diode technologies. => Sometimes the reason for external fast recovery diodes.



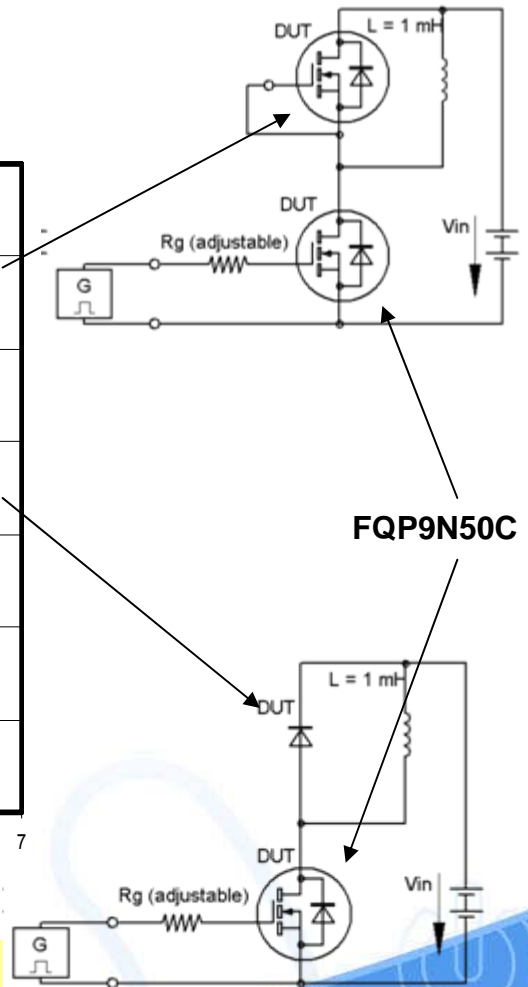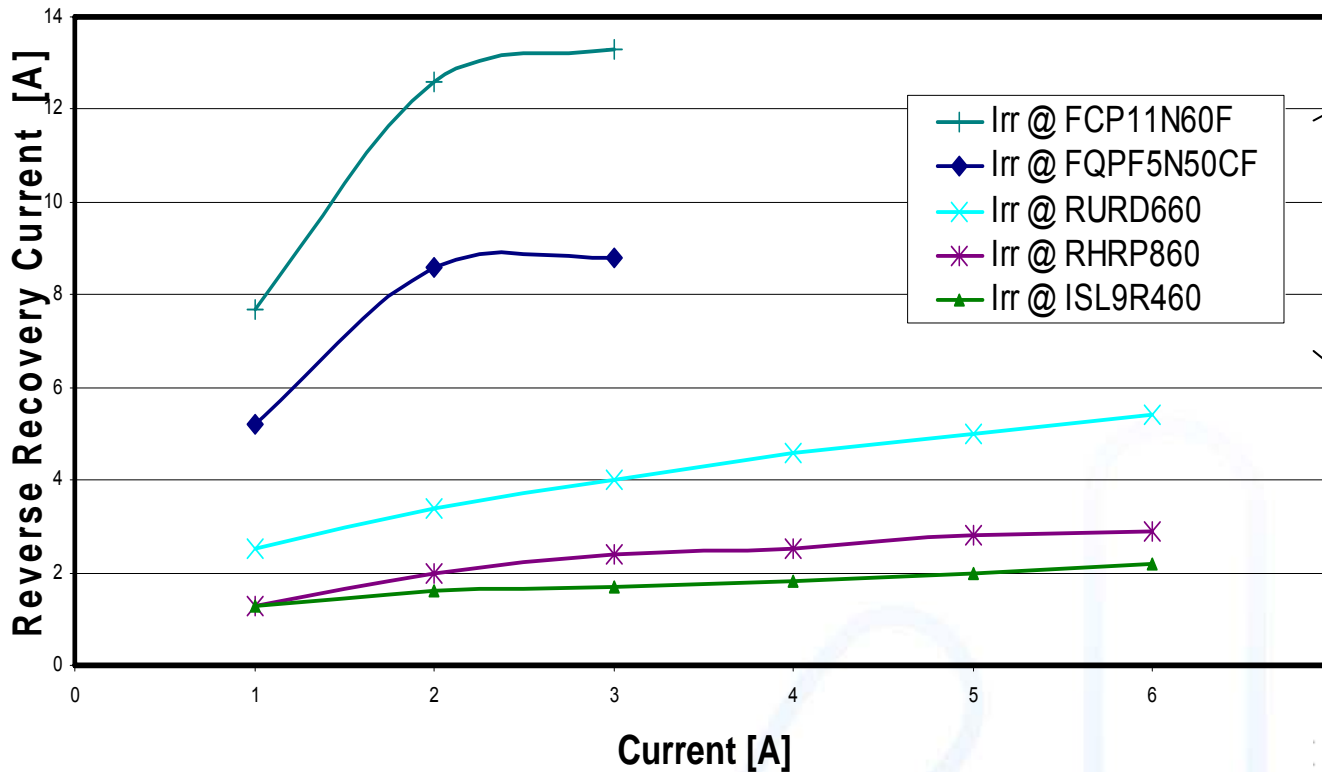I_{rr} , Reverse Recovery Peak Current of the Diode vs. Current




FQP9N50C


I_{rr} values are a good indicator for a loss comparison of diodes.

Only I_{rr} 's measured at the same di/dt are comparable!

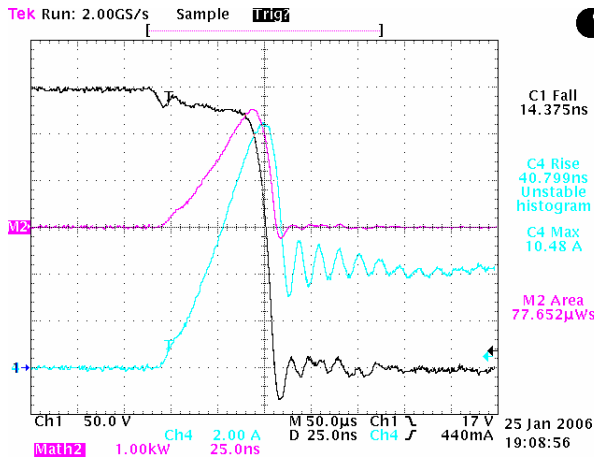
E_{ON} Losses at Hard Switching with different Diode Technology @ $V_{IN} = 300V$ @ $I = 4A$




MUR1560; $E_{ON} = 77.7\mu J$

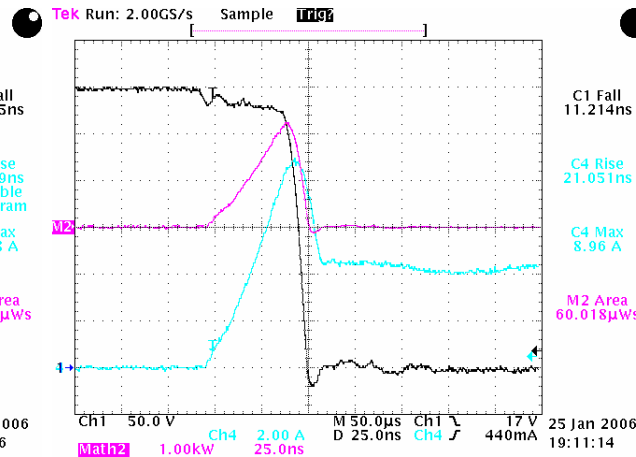


RURD660; $E_{ON} = 60.1\mu J$

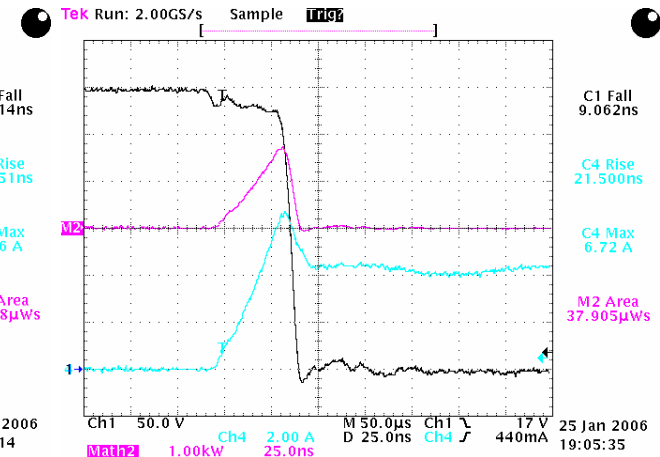


RHRP860; $E_{ON} = 37.9\mu J$

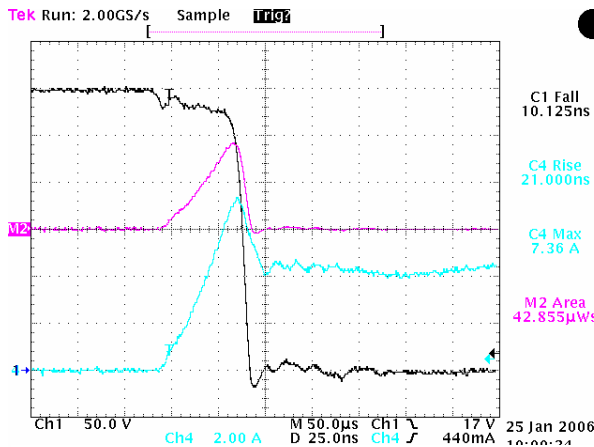

ISL9R1560; $E_{ON} = 42.9\mu J$


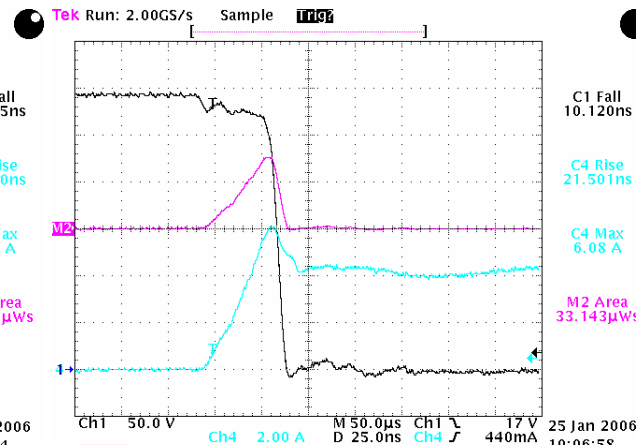


ISL9R860; $E_{ON} = 33.1\mu J$

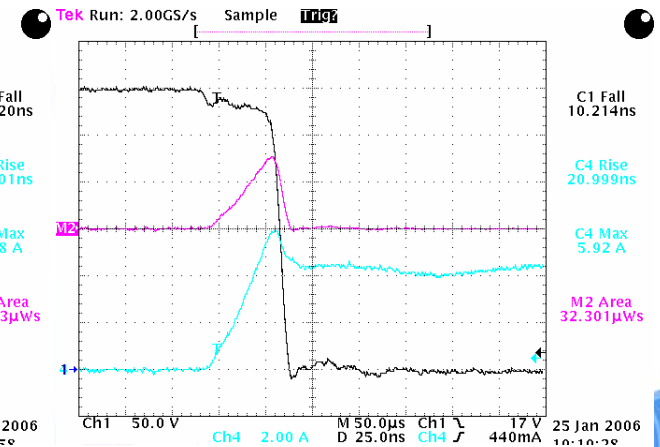

ISL9R460; $E_{ON} = 32.3\mu J$

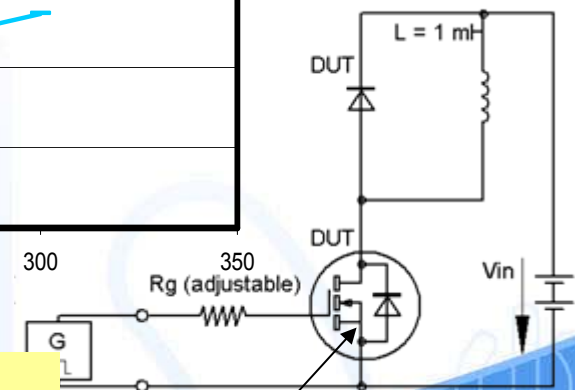
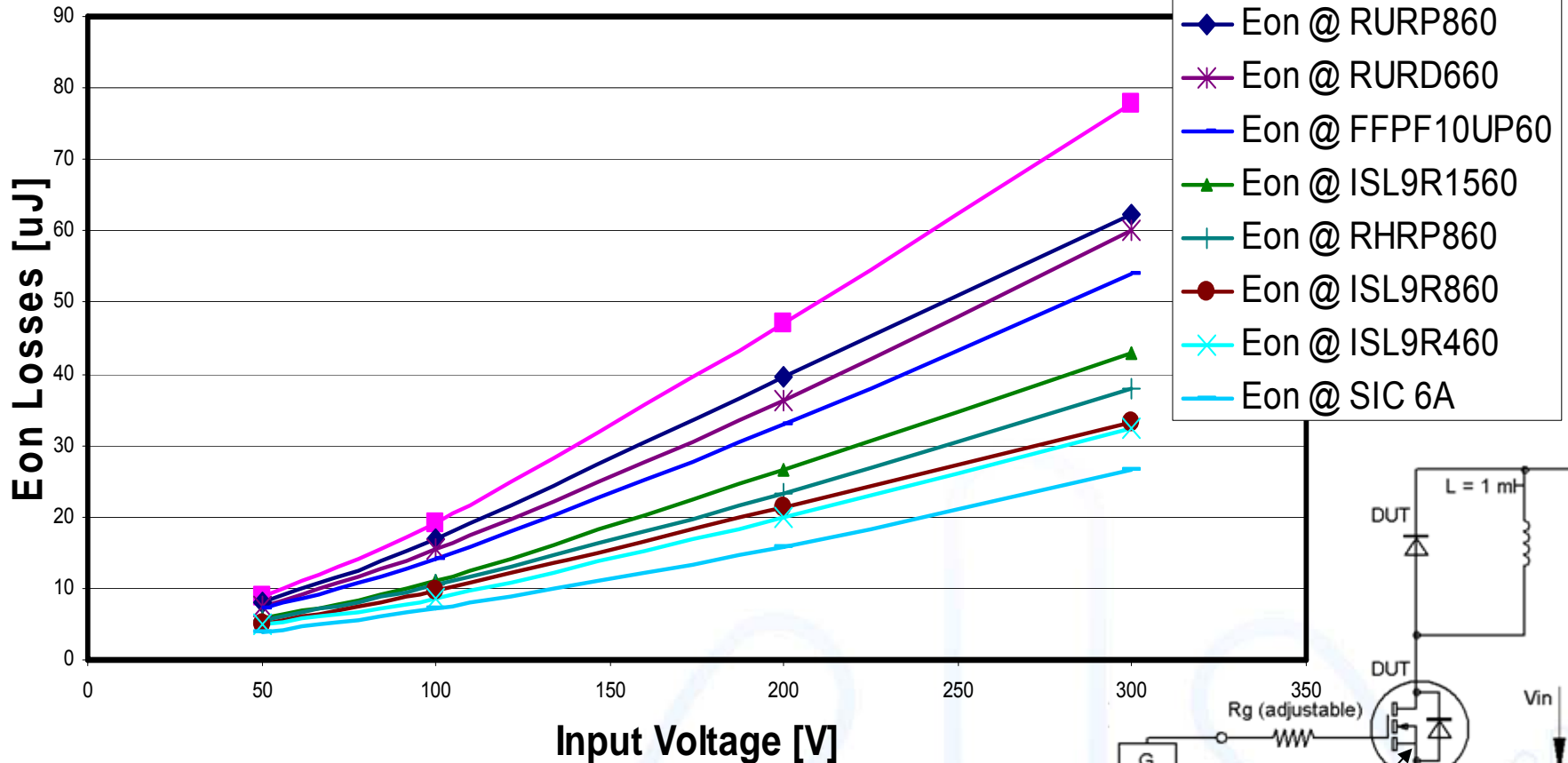
Eon losses of the FET - FQP9N50C vs. Input Voltage



Especially in hard switching applications the diode technology will have a significant impact on the E_{on} losses of the switch.

FQP9N50C

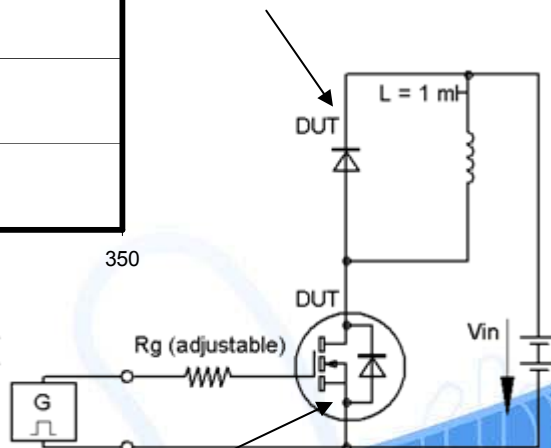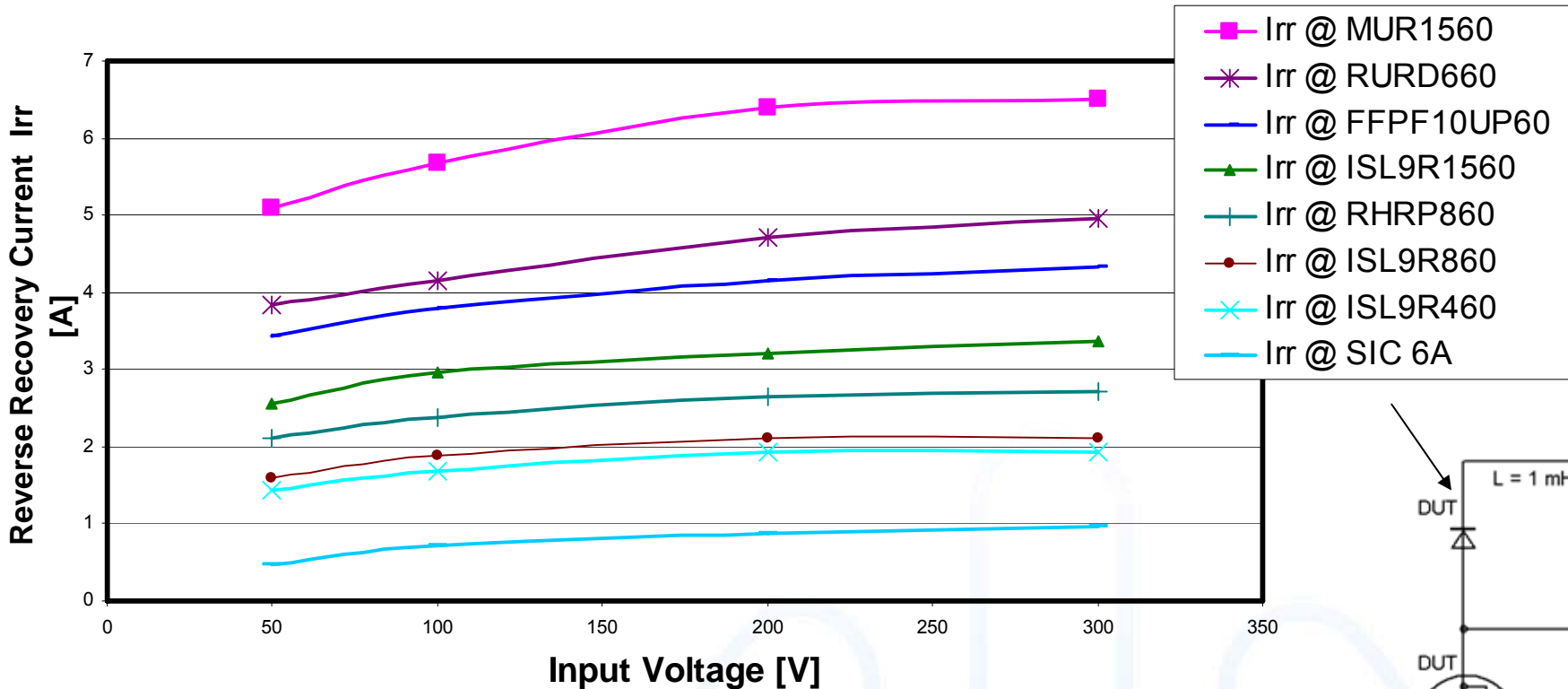I_{rr} , Reverse Recovery Peak Current of the Diode vs. Input Voltage




FQP9N50C

The I_{rr} value is a good parameter to estimate the switching losses of different technologies.

Only I_{rr} 's measured at the same di/dt are comparable!


$di/dt = 200A/ms$, $V_{dd} = 400V$, $I_f = 8A$, $T_j = 25^\circ C$ and $T_j = 125^\circ C$

Two industry standard diodes

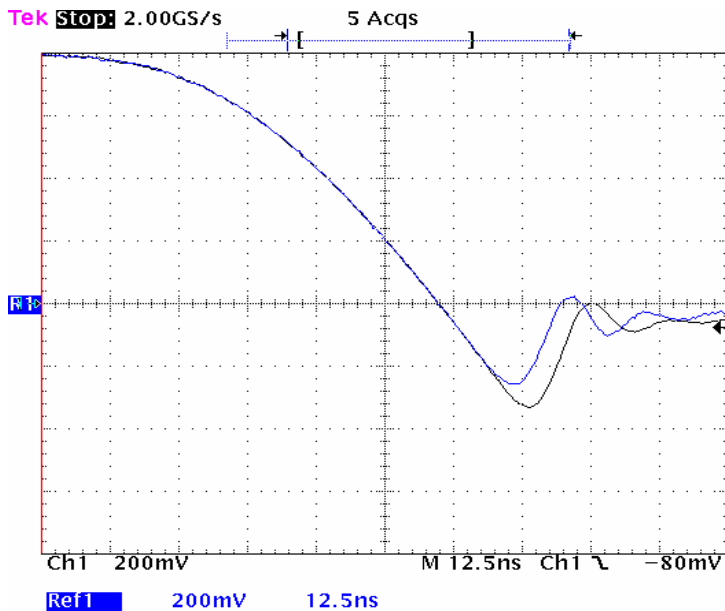

Results for $T_j = 25^\circ C$

Small difference

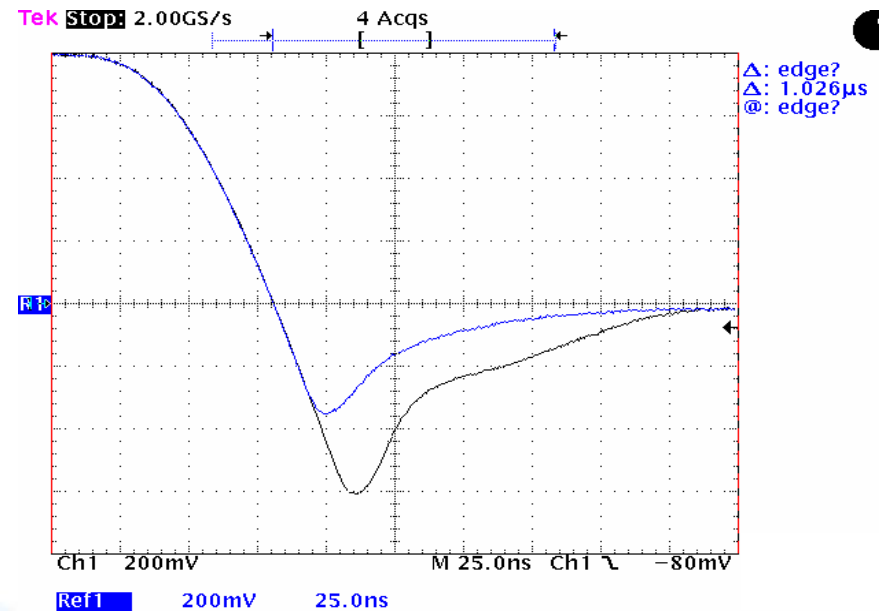

Results for $T_j = 125^\circ C$

Big difference

The difference between low and high temperature reverse recovery behavior is not the same for all technologies. Be careful if you compare only at low temperatures.



- Switching off:

Same FET and Diode, reducing R_g :

$$E_{OFF} = 22.8\mu J \Leftrightarrow 16.7\mu J$$


Drawback: ringing due to parasitic Ind. & Caps

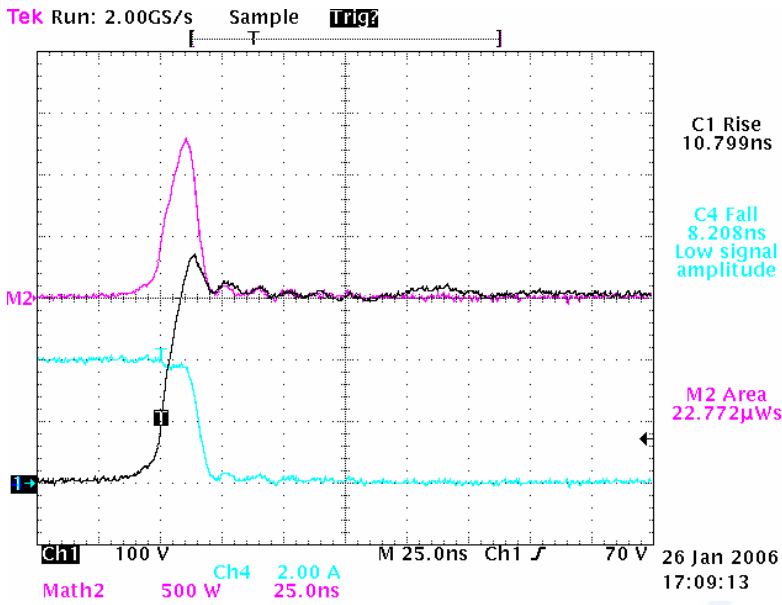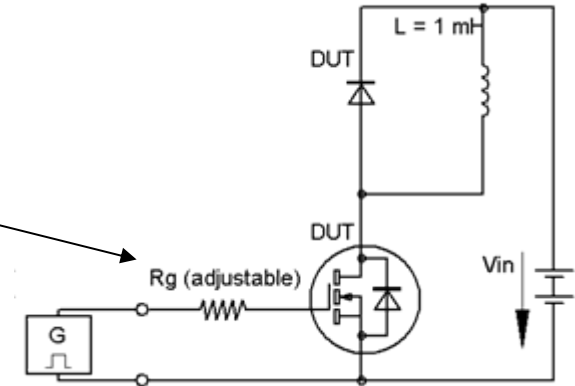All measurements: FDD6N50 + ISL9R460, $U = 300V$, $I = 4A$



Recommended R_g


Good switching performance, no ringing

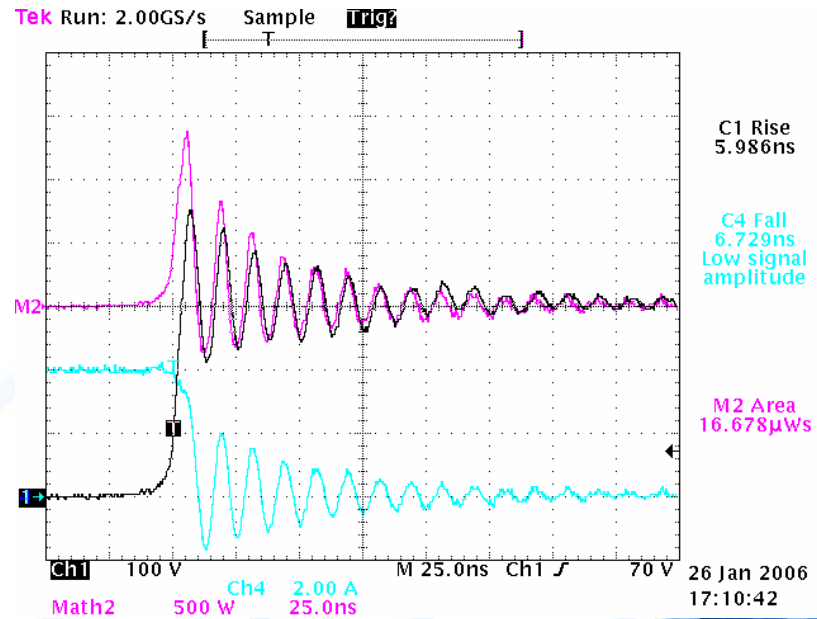

Low R_g

Bad switching performance, ringing, but lower E_{OFF}

Diode = ISL9R460, U = 300V, I = 4A

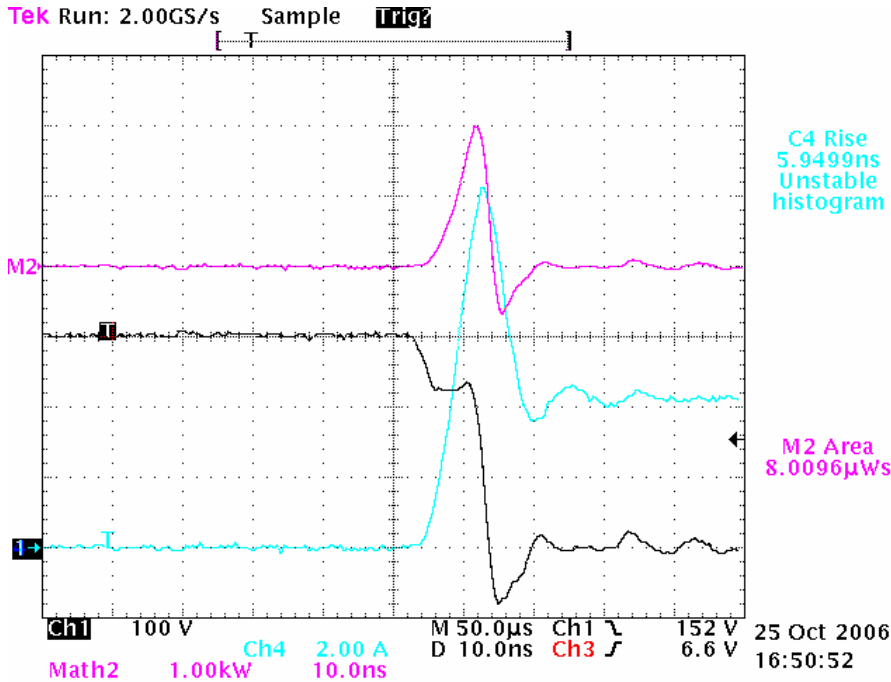


FDD6N50, Rg = 10 Ohm

$E_{ON} = 8 \text{ uJ}$

$di/dt = 1400\text{A/us}$

$I_{RRM} = 6.2\text{A}$

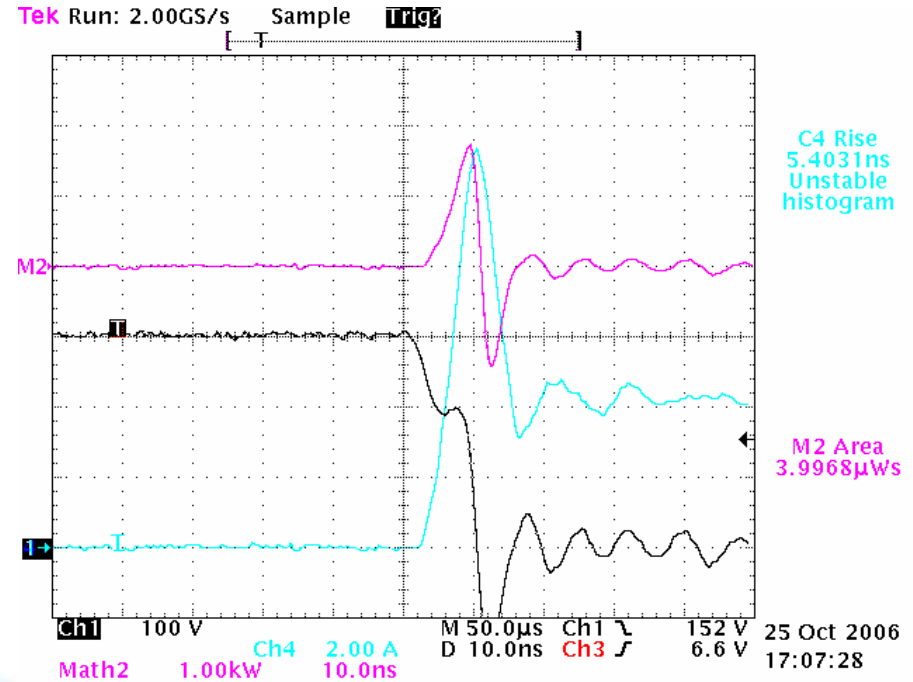


Right : FDD6N50, Rg = 3 Ohm

$E_{ON} = 4 \text{ uJ}$

$di/dt = 1600\text{A/us}$

$I_{RRM} = 7.4\text{A}$

Diode = ISL9R460, U = 300V, I = 4A

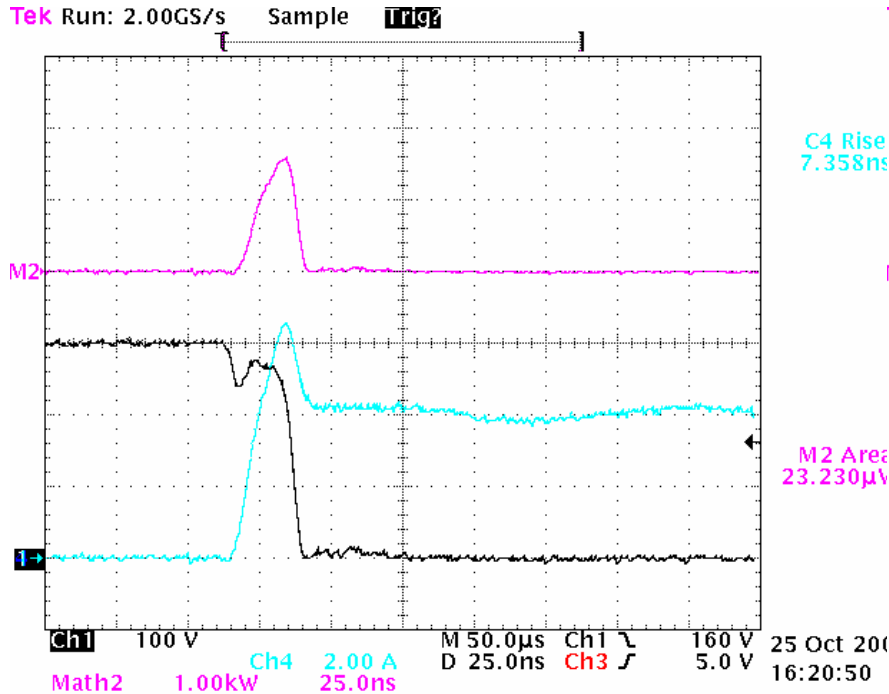


FQP9N50C, $R_g = 30 \text{ Ohm}$

$E_{ON} = 23.2 \text{ uJ}$

$di/dt = 400 \text{ A/us}$

$I_{RRM} = 2.6 \text{ A}$

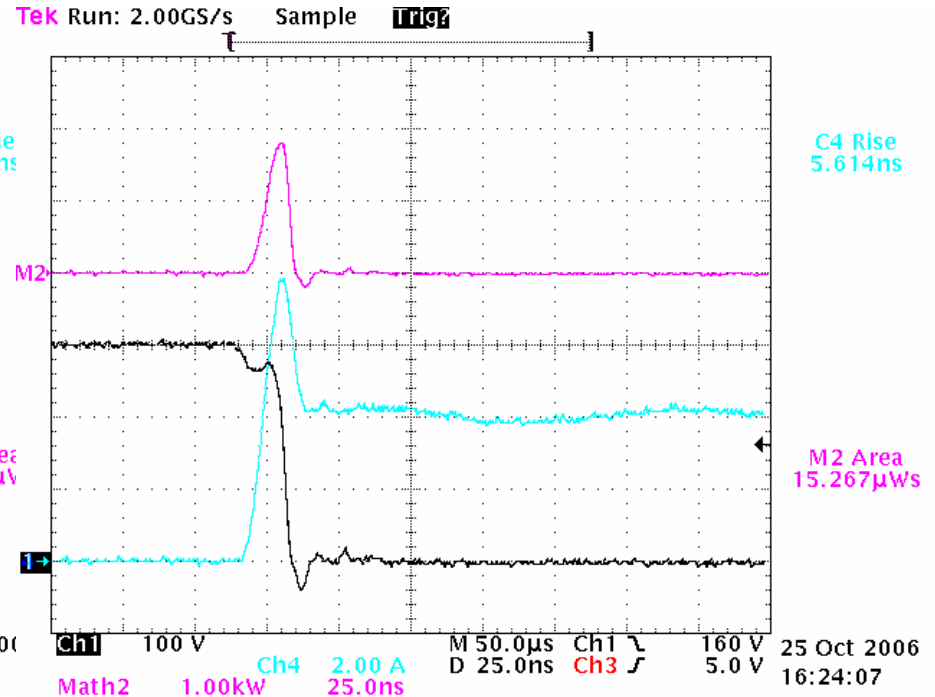


FDD6N50, $R_g = 30 \text{ Ohm}$

$E_{ON} = 15.3 \text{ uJ}$

$di/dt = 640 \text{ A/us}$


$I_{RRM} = 3.9 \text{ A}$

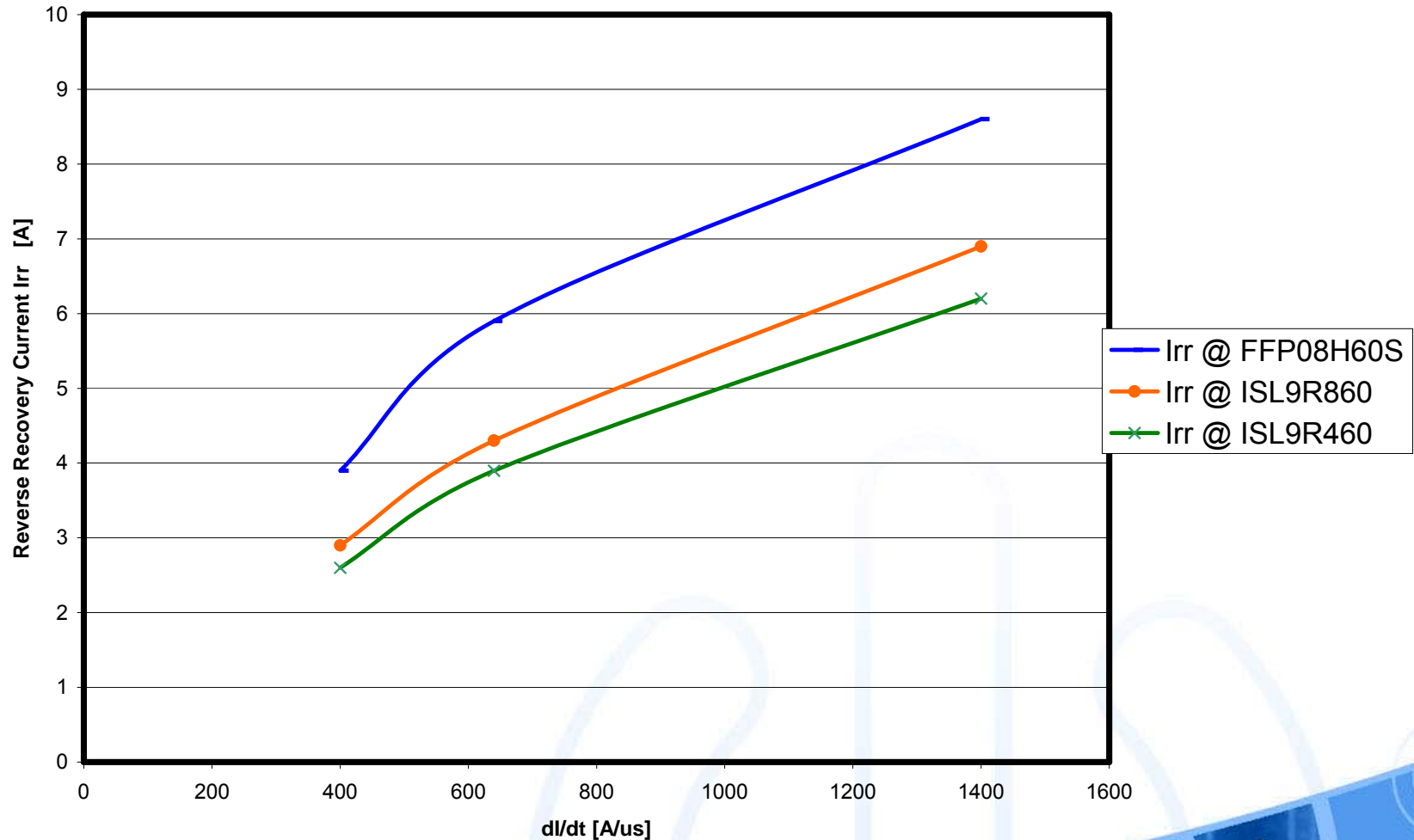Reverse Recovery Current I_{rr} of the Diode vs. di/dt @ $V = 300V$ @ $I = 4A$






A higher di/dt will increase the reverse recovery current, but...

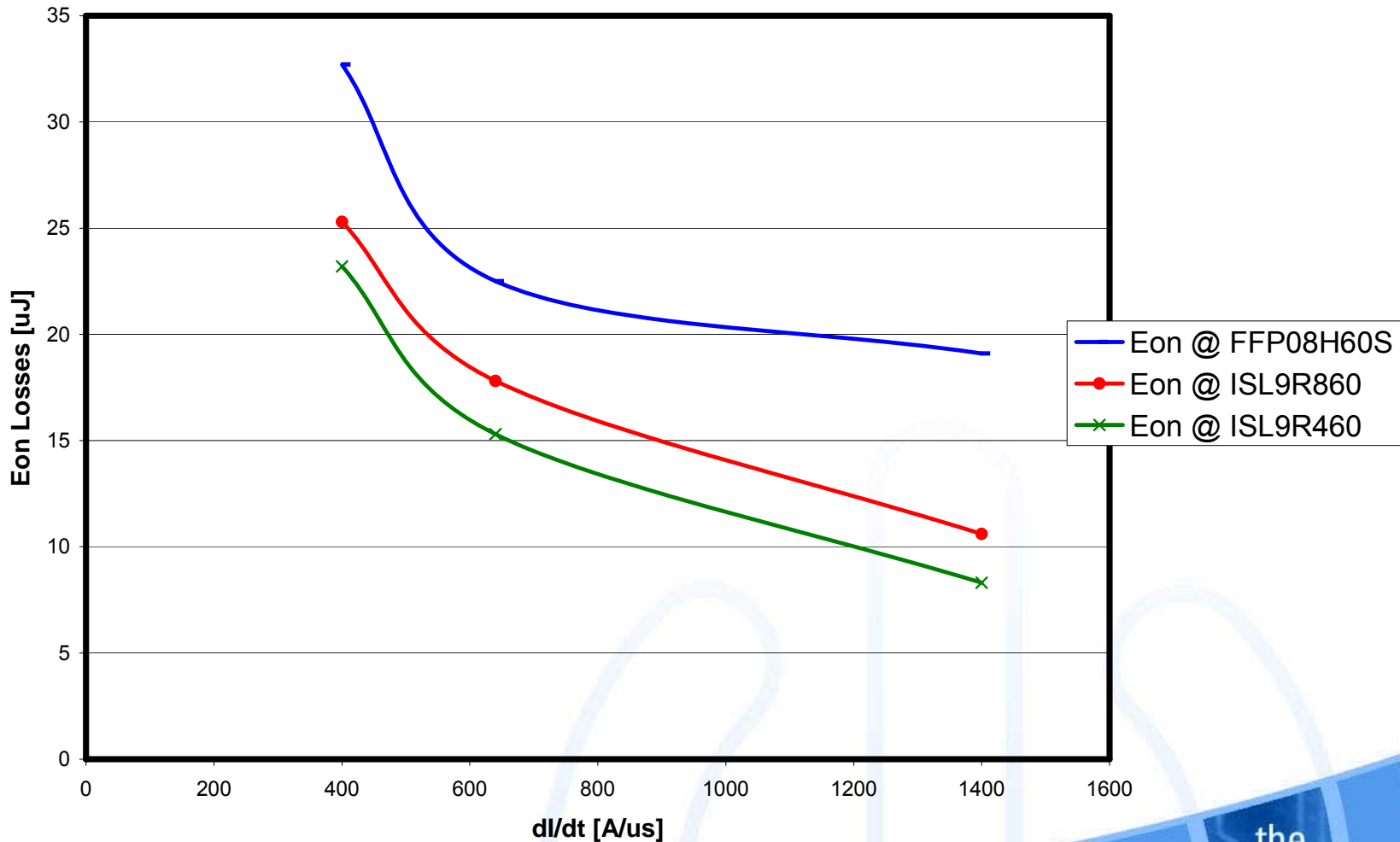Eon losses of the FET vs. di/dt @ $V = 300V$ @ $di/dt = 4A$



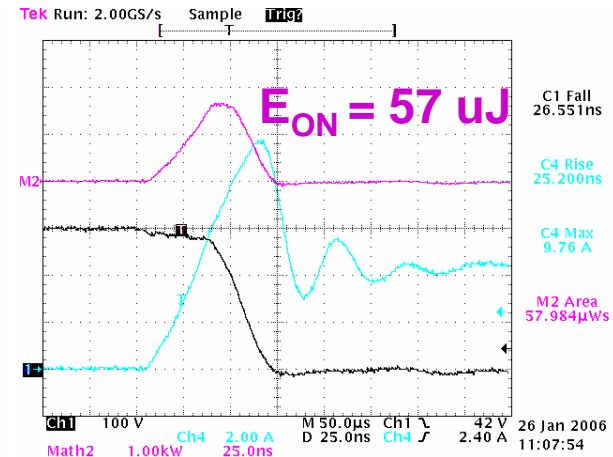
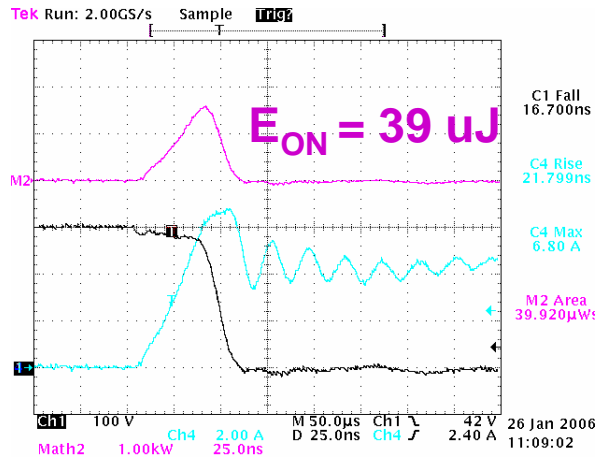
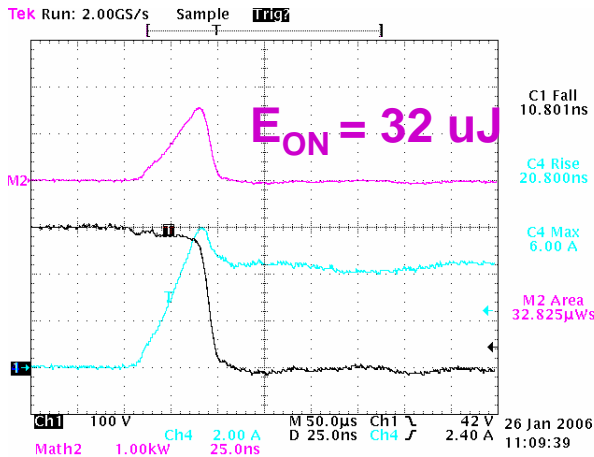
A higher di/dt will decrease the Eon losses.



No parallel Capacitance


Cpar = 470pF

Cpar = 1nF

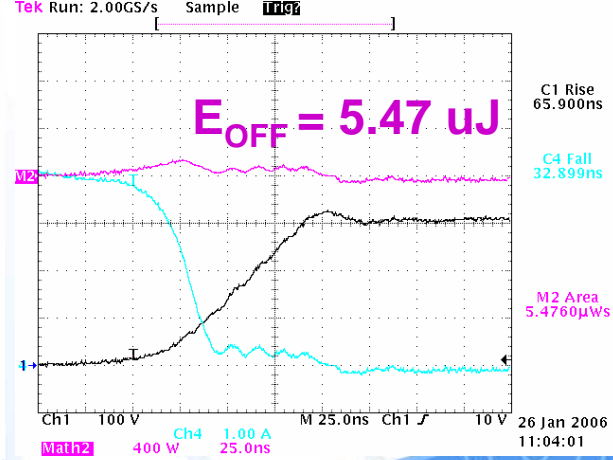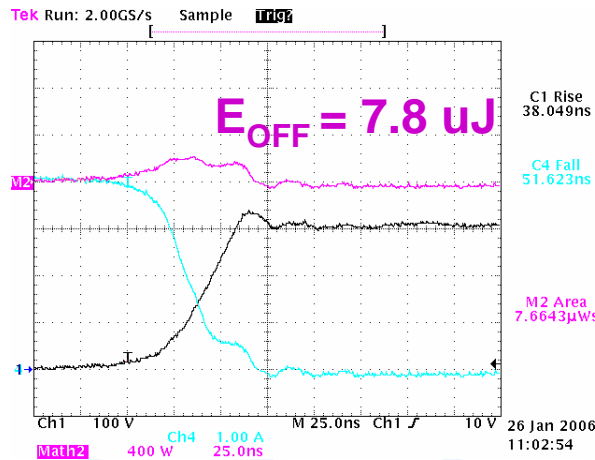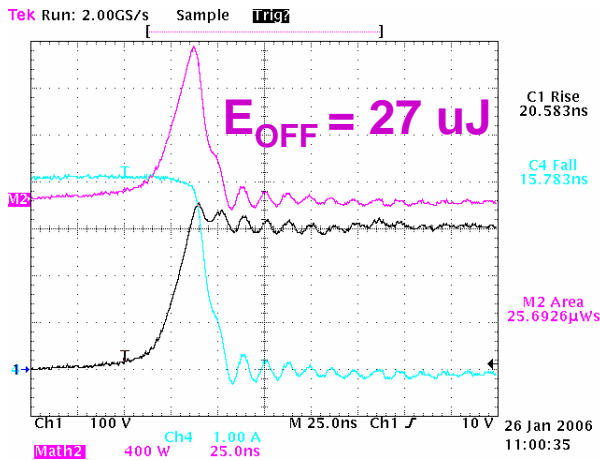

- Increase of the Eon losses due to the parallel Capacitance.
- Advantages in switching off
- Overall losses? ...

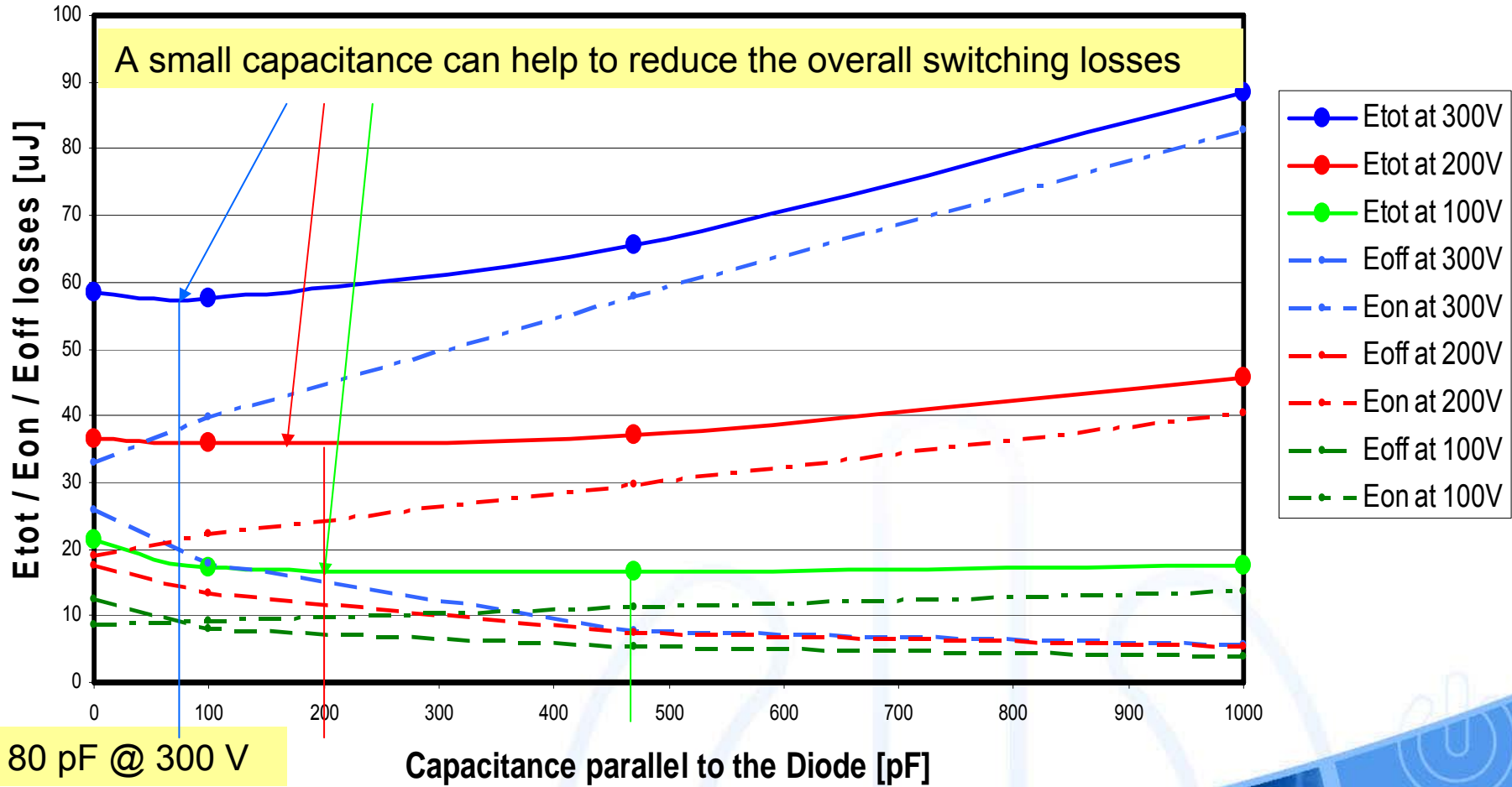Eon and Eoff losses with a snubber Capacitance



As higher the voltage, as smaller the cap to decrease the overall losses.

- Reverse recovery in diodes in half-bridge structures causes
 - small losses in the diodes
 - larger losses in the MOSFET/IGBT

- I_{RRM} and t_{RR} increase with
 - temperature
 - di/dt
 - current (less dominant)

- Larger current rated diodes of the same family
 - have higher I_{RRM} resulting in higher E_{ON} (measured at the same di/dt for comparison)
 - have larger capacitance, resulting in lower E_{OFF}
 - cause higher total switching losses

- Higher di/dt results in lower E_{ON} losses, but also in a higher I_{RRM}

- Addition of extra capacitance
 - increases E_{ON} losses but decreases E_{OFF} losses
 - addition of extra capacitance could reduce total losses.