

Hardware Description Languages

- VHDL
 - VHSIC (Very High Speed Integrated Circuit) Hardware Description Language
 - Taught in EEC 180B
- Verilog
 - Generally more common in industry
 - Similarities with C

HDL

- Hardware Description Language
- Design process
 - Think
 - Draw diagram of hardware, figure out where logic and registers go
 - Think
 - Then...
 - Write verilog
 - Test it

HDL

- You'll write far better HDL code if you think of it differently than a standard programming language
 - a way to code an *algorithm*
- Hardware description language
 - a way to code *hardware!*

HDL Simulation Tools


- Synopsys
 - VCS – simulator
 - Virsim – waveform viewer and environment
- Cadence
 - Verilog XL – simulator
 - NC Verilog – simulator
 - Simvision – waveform viewer and environment
- Many others...

Verilog

- *Modules* are basic building blocks
- Main ways to do logic
 - *wires, assign* statements
 - *registers, always* blocks

wire, assign

 
- Picture “always active” hardwired logic
- Declare all wires



wire, assign

- Example:


```
wire out;  
assign out = a & b;
```

 

wire, assign

 - Example:

```
wire out;  
assign out = sel ? b : a;
```



reg, always


- Picture a much more general way of assigning “wires” or “nodes”
- Use “if/else” and “case” statements
- Can, but don’t use “for loops” in logic blocks (ok for testing code)
- Procedural execution – statements execute in order

reg, always

 - Example:

```
reg out;  
always @(a or b) begin  
    out = a & b;  
end
```


“Sensitivity list” declares when to execute the code within the *always* block.



reg, always

 - Example:

```
reg out;  
always @(a or b) begin  
    out = a & b;  
end
```



Operation goes like this:


Anytime *a* or *b* changes, re-evaluate *out = a & b*; otherwise, keep *out* the same.

Notice that there is the possibility of a problem (memory) if all inputs are not included in the sensitivity list.

wire, assign

 - Example:


```
reg out;  
always @(a or b or sel) begin  
    if (sel == 1'b1) out = b;  
    else out = a;  
end
```



reg, always

- Building a flip-flop
 
```
reg Q;
always @(posedge clock) begin
    Q = D;
end
```
- The only time the flip-flop output Q gets updated is at the positive edge of the clock signal -> exactly what we want for a flip-flop.




Concurrent Operation

- You can think of these as operating on independent circuits (remember *hardware* orientation).

```
always begin
    x = a & b;
    #5;          // 5-unit delay
end
```
 
```
always begin
    y = ~(b ^ c);
    #7;          // 7-unit delay
end
```



- Both functions compute during the same "simulation" time, just as with real hardware

Typical Design Flow

- Synthesis tool converts HDL into a netlist of appropriate components
 - FPGA: “CLB” or “slice” components
 - Custom chip: standard cells

