


# Lecture 25

- Last time:
  - Cascode: merged CS/CG cascade
  - Cascode current supplies
- Today :
  - Cascode transconductance amplifier: full design

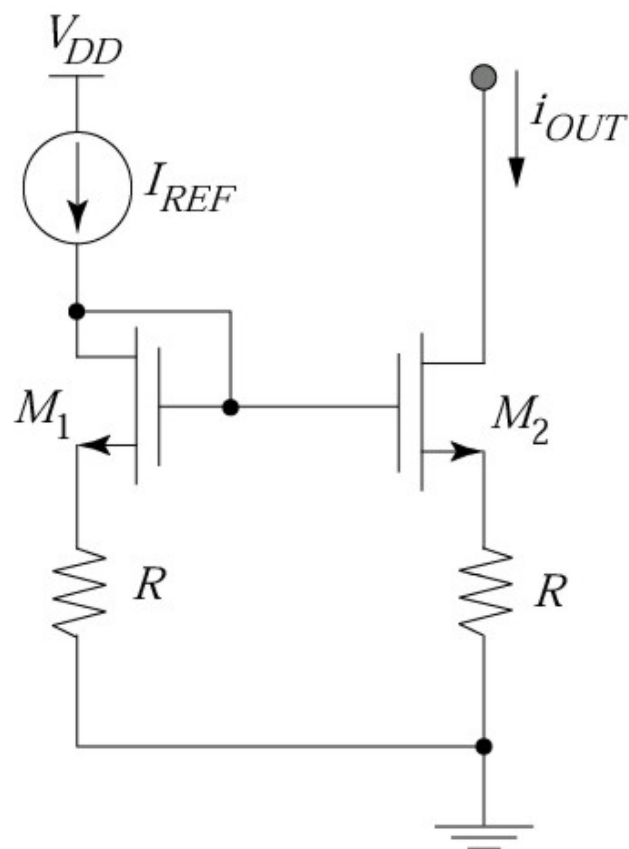
# Improved Current Sources

Goal: increase  $r_{oc}$

Approach: look at *amplifier* (?) output resistance results  
... to see topologies that boost resistance



# Cascode (or Stacked) Current Source

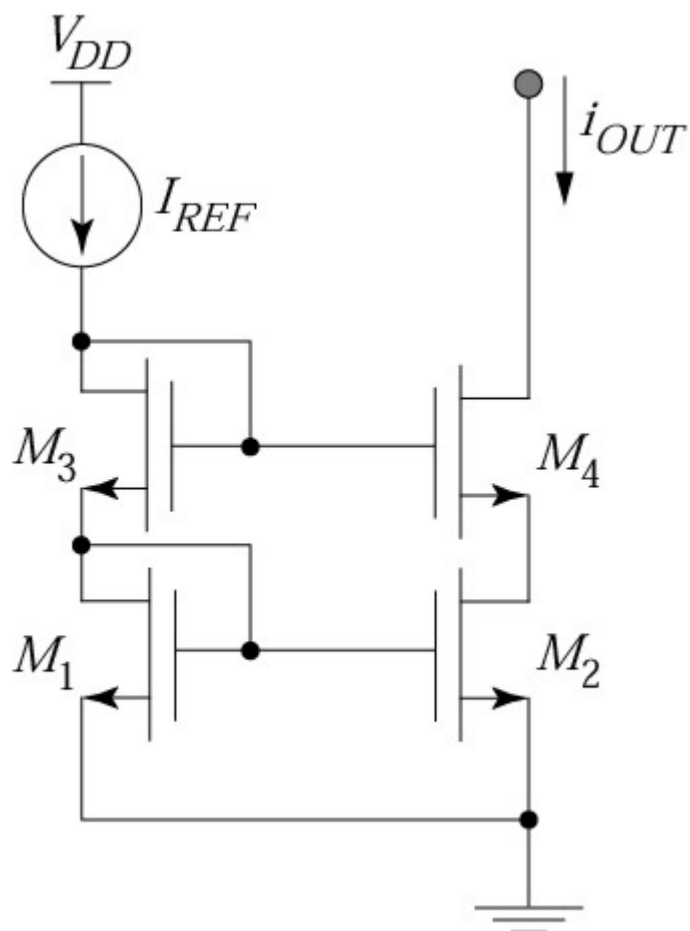

Insight:  $V_{GS2} = \text{constant}$  AND  
 $V_{DS2} = \text{constant}$

Small-Signal Resistance  $r_{oc}$ :

# Drawback of Cascode $I$ -Source


Minimum output voltage for all transistors saturated:

$$V_{OUT,MIN} = V_{DS4,SAT} + V_{S4} = V_{DS4,SAT} + V_{GS2}$$


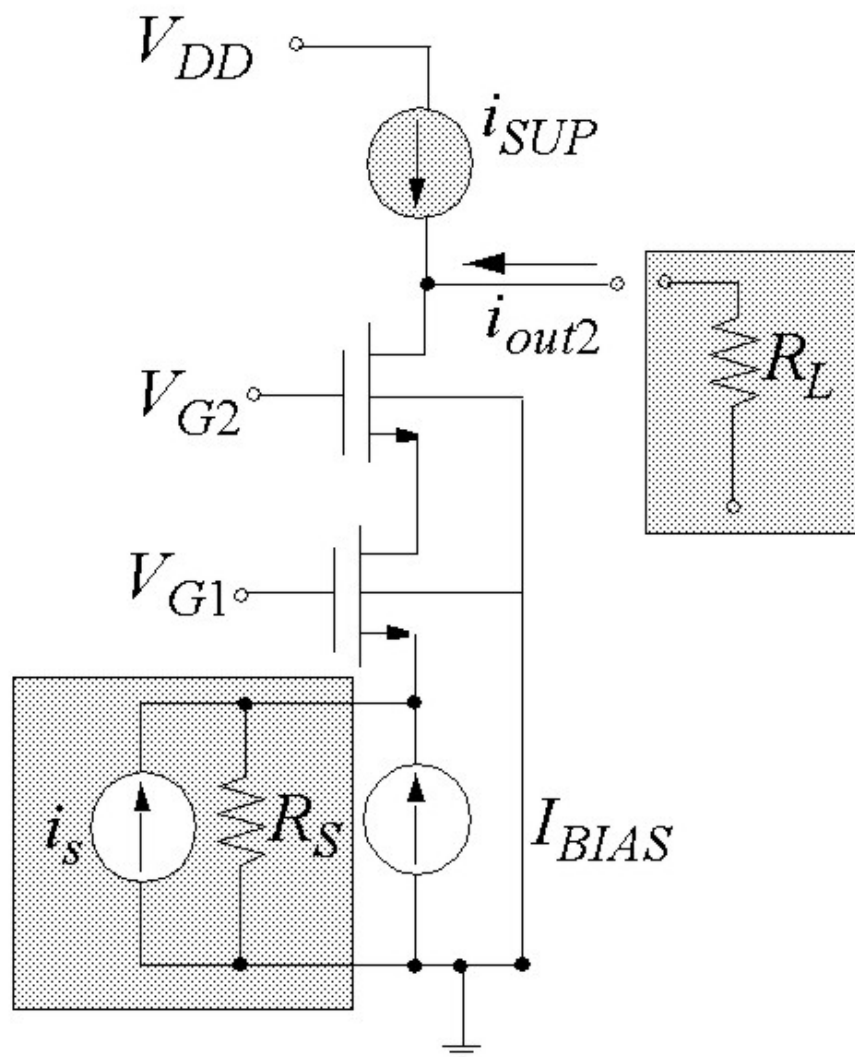
# CG Cascade: Sharing a Supply

First stage has no current supply of its own  $\rightarrow$  its output resistance is modified




# Amplifier Topology

Goals:  $R_{in}$  and  $R_{out}$  should be maximized

Common source – common gate cascode makes sense


Share the current supply

# Amplifier Schematic

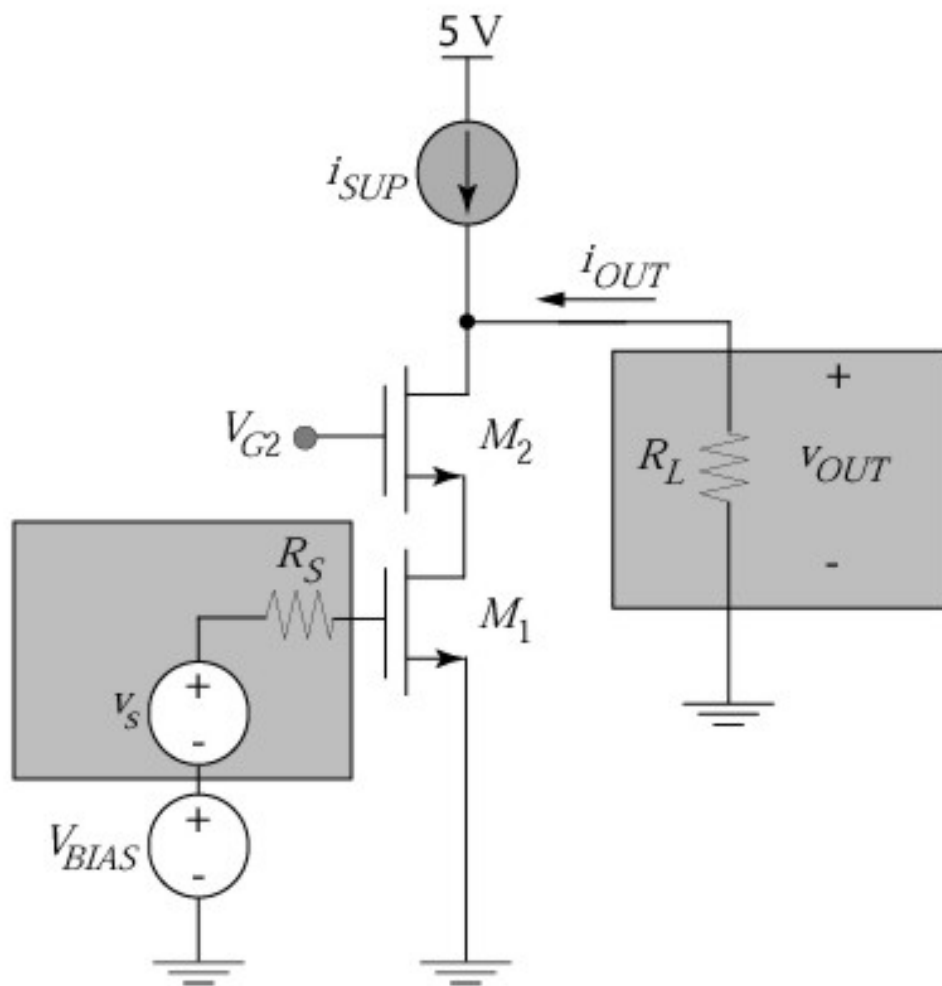

Note that the backgate connection for  $M_2$  is not specified: ignore  $g_{mb}$

# Current Supply Design

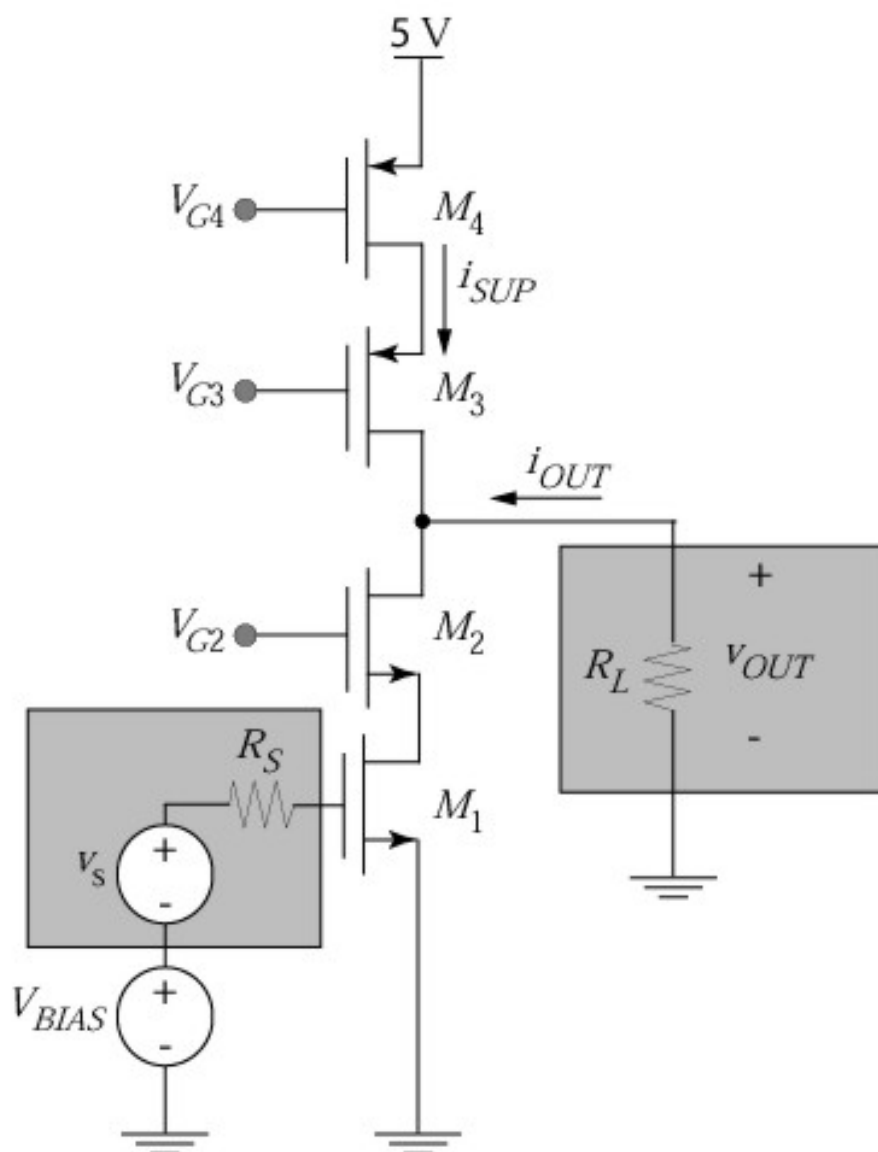


Output resistance goal  
requires large  $r_{oc}$   $\rightarrow$   
use cascode current source



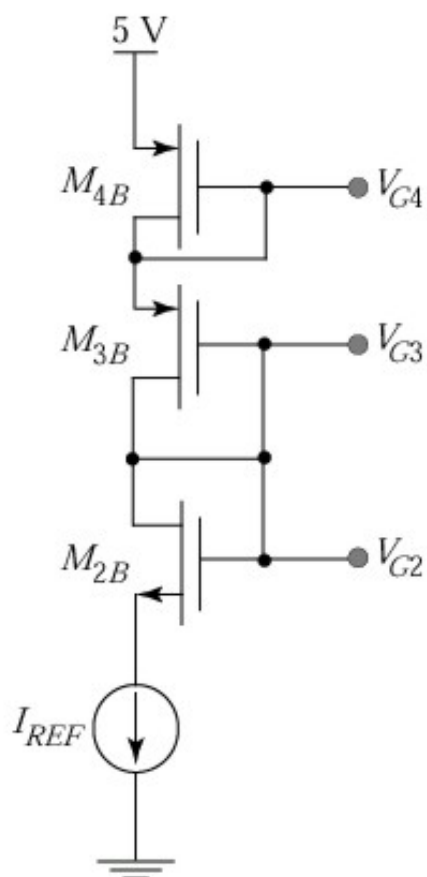
# Totem Pole Voltage Supply

DC voltages must be set for the cascode current supply transistors  $M_3$  and  $M_4$ , as well as the gate of  $M_2$ .



Why include  $M_{2B}$ ?

# Complete Amplifier Schematic

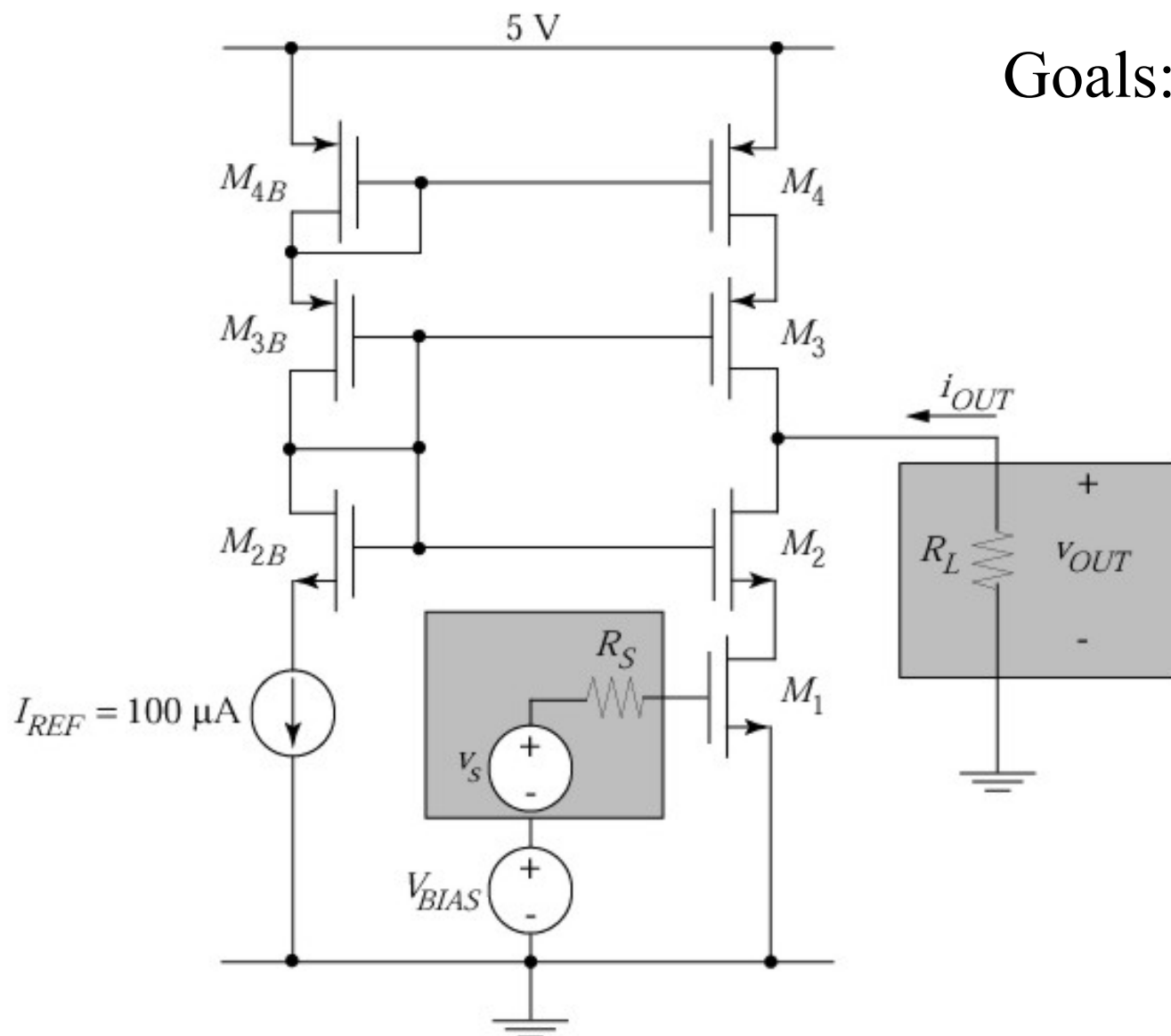

Goals:  $g_{m1} = 1 \text{ mS}$ ,  
 $R_{out} = 10 \text{ M}\Omega$

# Device Sizes

$M_1$ : select  $(W/L)_1 = 200/2$  to meet specified  $g_{m1} = 1 \text{ mS}$   
 $\rightarrow$  find  $V_{BIAS} = 1.2 \text{ V}$


Cascode current supply devices: select  $V_{SG} = 1.5 \text{ V}$   
 $(W/L)_4 = (W/L)_{4B} = (W/L)_3 = (W/L)_{3B} = 64/2$

$M_2$ : select  $(W/L)_2 = 50/2$  to meet specified  $R_{out} = 10 \text{ M}\Omega$   
 $\rightarrow$  find  $V_{GS2} = 1.4 \text{ V}$

Match  $M_2$  with diode-connected device  $M_{2B}$ .

Assuming perfect matching and zero input voltage,  
 what is  $V_{OUT}$ ?

# Output (Voltage) Swing

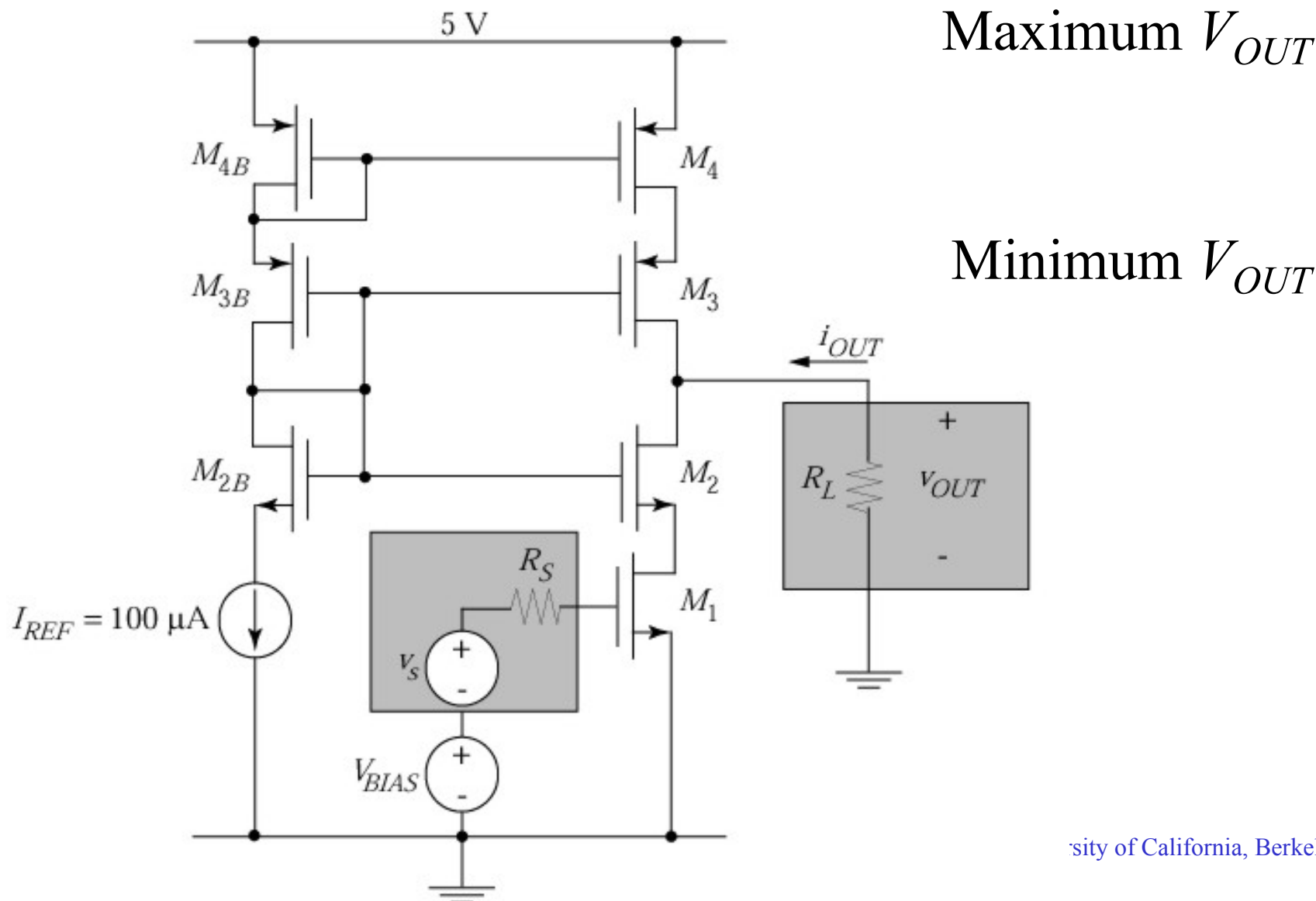

# Two-Port Model

Find output resistance  $R_{out}$

$$\lambda_n = (1/20) \text{ V}^{-1}, \lambda_n = (1/50) \text{ V}^{-1} \text{ at } L = 2 \mu\text{m} \rightarrow$$

$$r_{on} = (100 \mu\text{A} / 20 \text{ V}^{-1})^{-1} = 200 \text{ k}\Omega, r_{op} = 500 \text{ k}\Omega$$

$$g_{m2} = \frac{2I_{D2}}{V_{GS2} - V_{Tn}} = \frac{2(100 \mu\text{A})}{1.4\text{V} - 1\text{V}} = 500 \mu\text{S}$$

$$g_{m3} = \frac{2(-I_{D3})}{V_{SG3} + V_{Tp}} = \frac{2(100 \mu\text{A})}{1.5\text{V} - 1\text{V}} = 400 \mu\text{S}$$

$$R_{out} = r_{oc} \parallel r_{o2} (1 + g_{m2} R_{S2}) = r_{o3} (1 + g_{m3} R_{S3}) \parallel r_{o2} (1 + g_{m2} r_{o1})$$

# Voltage Transfer Curve

Open-circuit voltage gain:  $A_v = v_{out} / v_{in} = -g_{m1}R_{out}$

