



# Operational Amplifiers



ME 6405, Fall '04

---

---

Martin Gudem

Nurudeen Olayiwola

Henry Won

# ▶ Operational Amplifiers ◀


---

---


Goals :

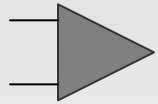- Introduction
- Characteristics
- Types
- Models VS. reality






# Introduction

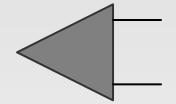


Most transducers provide analog signals:

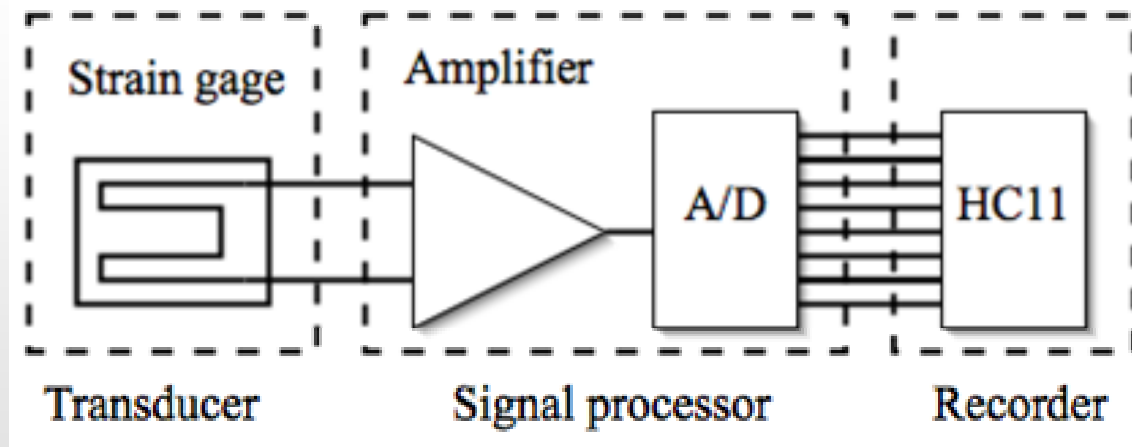
- Too small
- Too noisy
- Wrong information
- DC offset



Measurement system

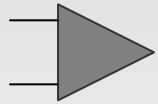

# Amplifiers

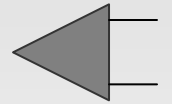



- Ideally: Increase amplitude without affecting other properties of the signal
- Voltage gain:

$$A_v = \frac{V_{out}}{V_{in}}$$



- Impedances:
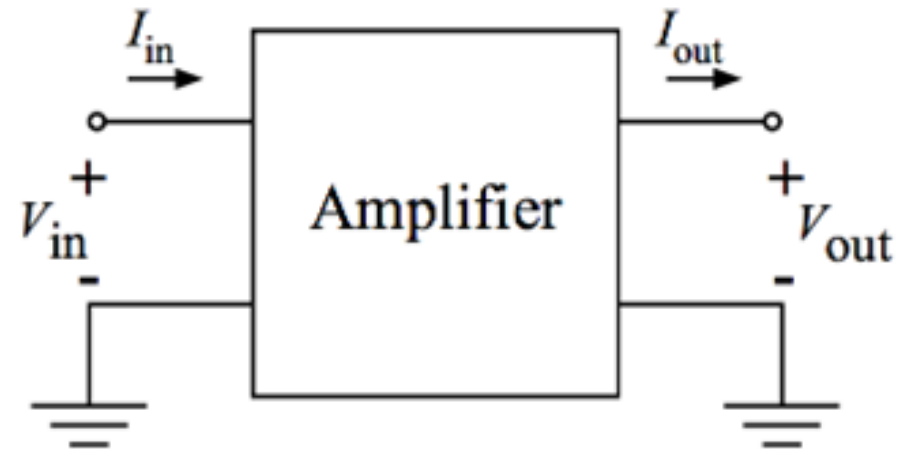
$$Z_{in} = \frac{V_{in}}{I_{in}} \quad Z_{out} = \frac{V_{out}}{I_{out}}$$




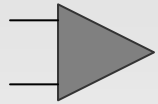


# Terminology

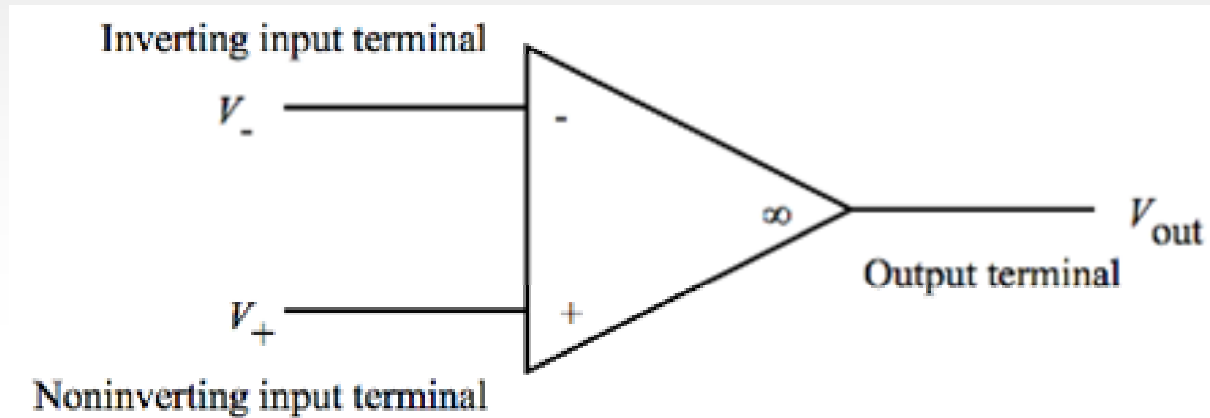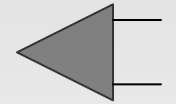


Open loop

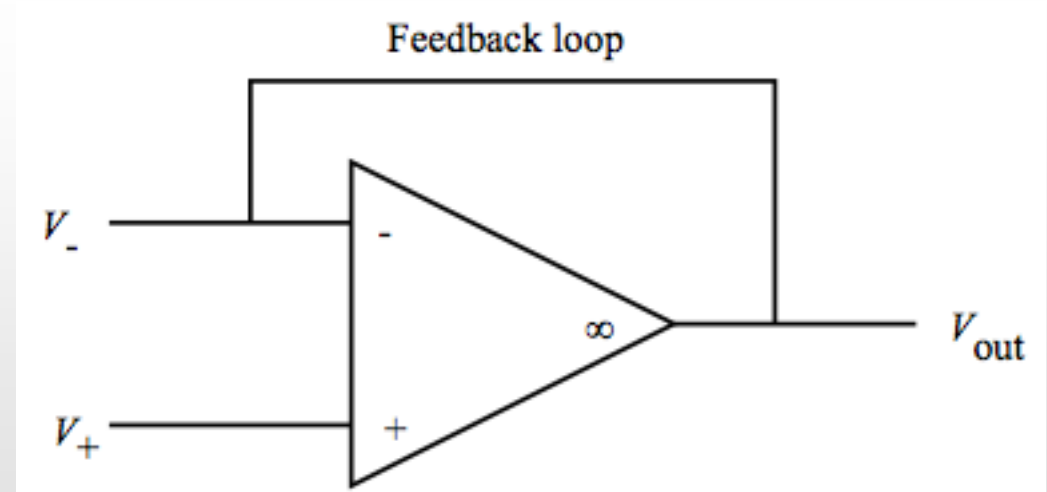

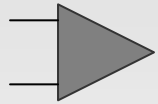
Closed loop  $\rightarrow$  Stabilized signal<sup>5</sup>




# Ideal Model

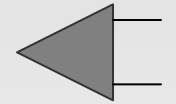


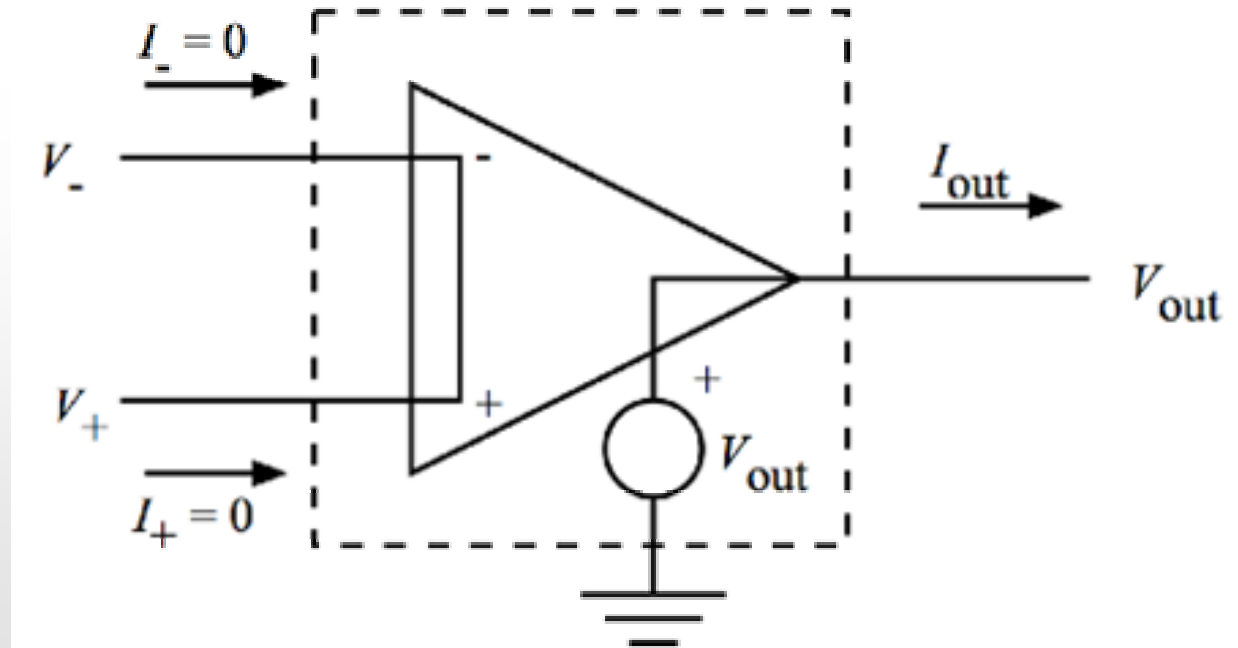- Aid in circuit analysis
1.  $I_+ = I_- = 0$
  2.  $V_+ = V_-$
  3.  $Z_{out} = 0$




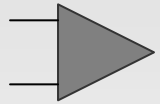


# Configuration

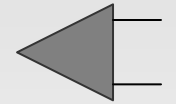





- 741 General purpose amplifier

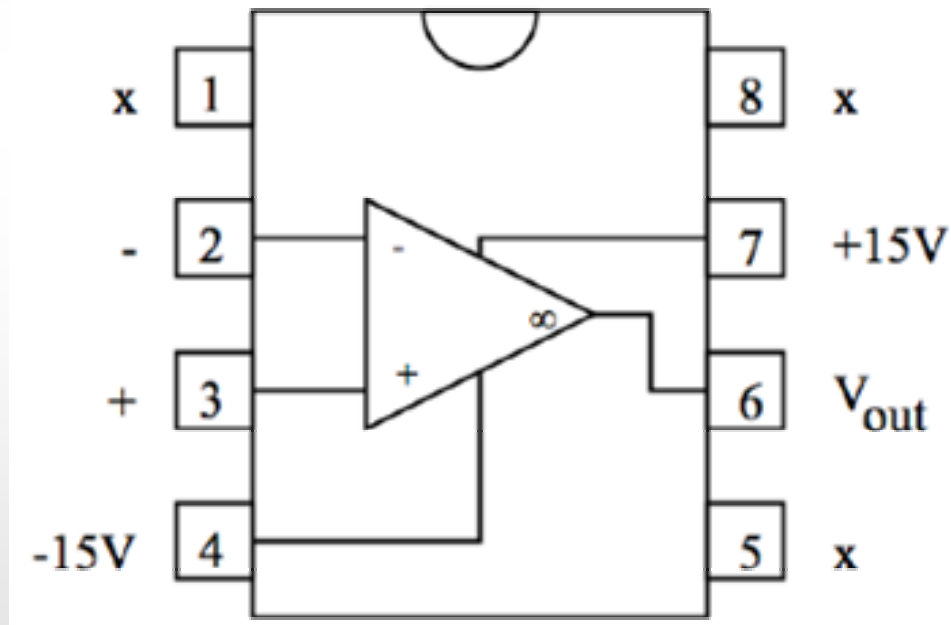


Pin-out

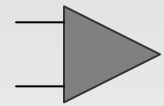


# Internal design

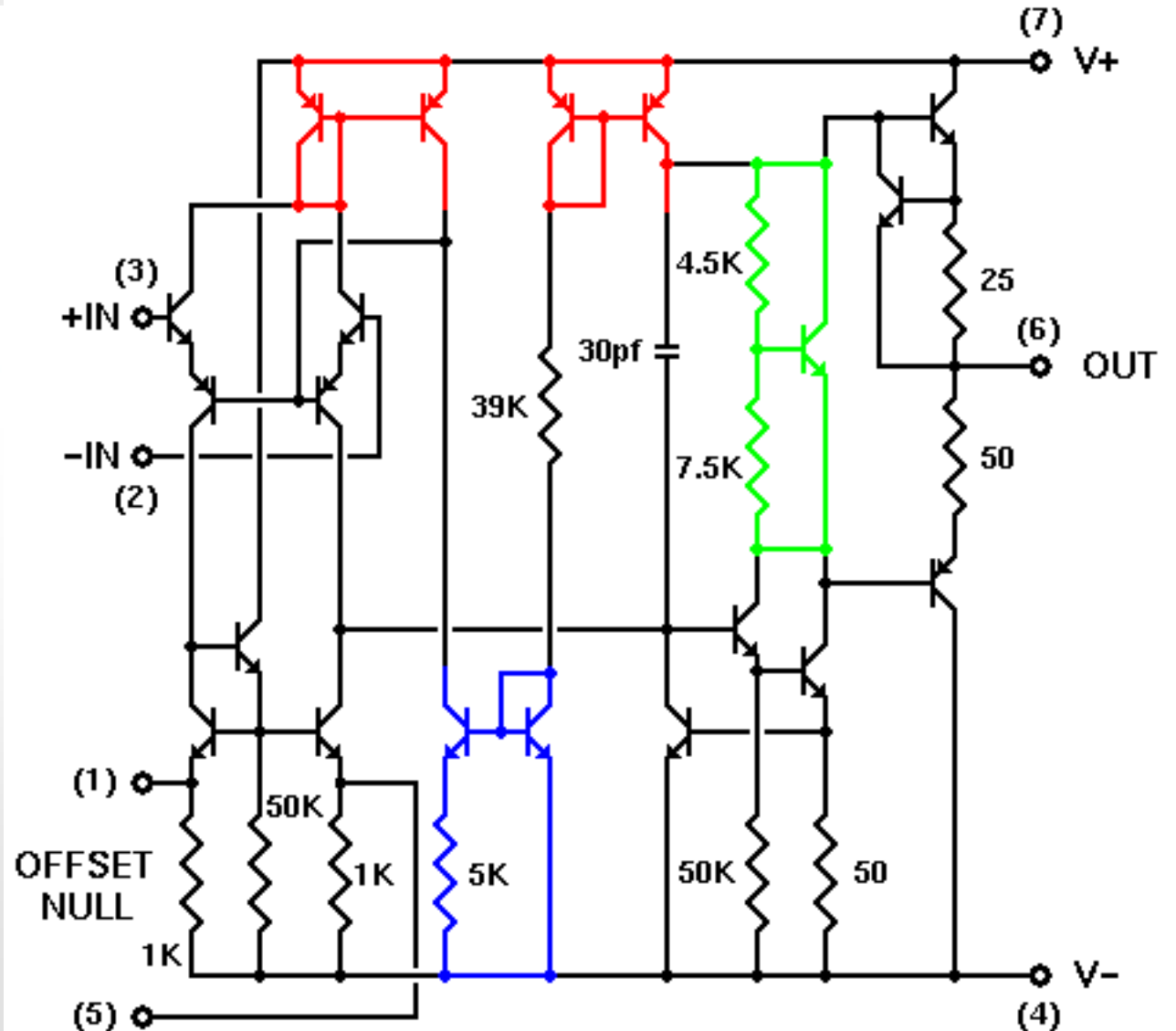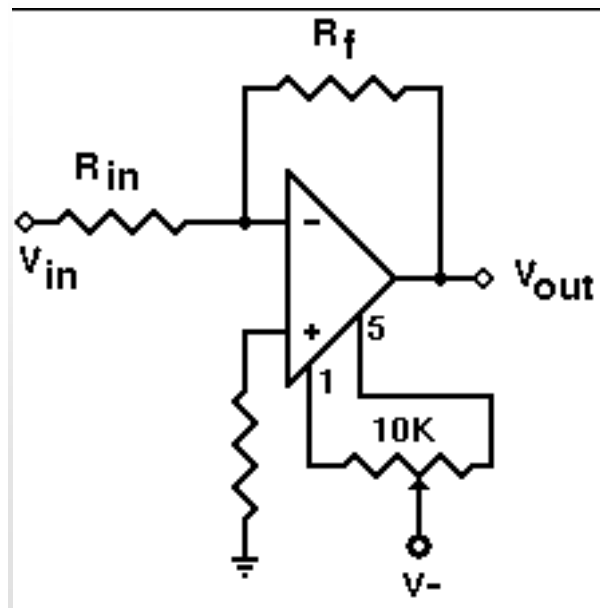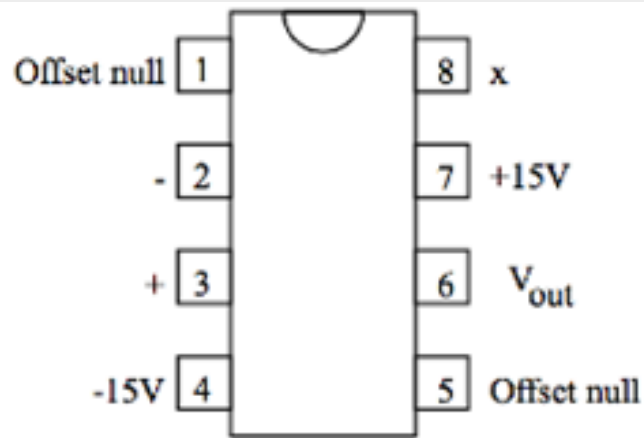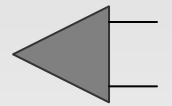





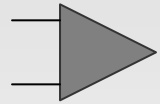

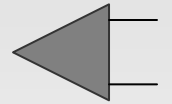

# The Ideal Op-Amp

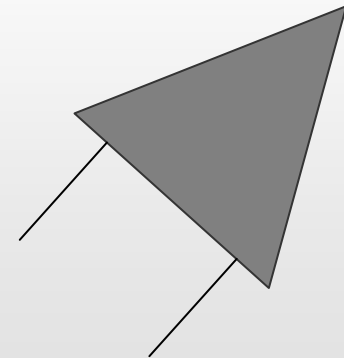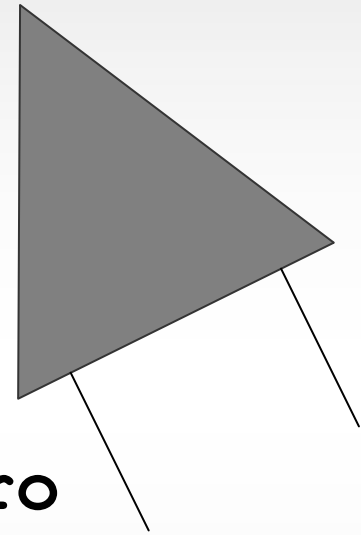


- Infinite Input Resistance
- Zero input current
- Zero Output Resistance
- Infinite Gain
- Common Mode Voltage Gain Zero
- Zero Noise / Zero Output Allowed
- Unlimited Bandwidth
- Temperature Independent




# ► Ideal v. Real Op-Amps ◀

	Ideal Op-Amp 	Typical Op-Amp 
Input Resistance	infinity	$10^6 \Omega$ (bipolar) $10^9 \Omega - 10^{12} \Omega$ (FET)
Input Current	0	$10^{-12} - 10^{-8} \text{ A}$
Output Resistance	0	100 - 1000 $\Omega$
Operational Gain	infinity	$10^5 - 10^9$
Common Mode Gain	0	$10^{-5}$
Bandwidth	infinity	Attenuates and phases at high frequencies (depends on slew rate)
Temperature	independent	Bandwidth and gain

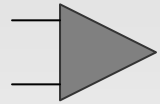
<http://hyperphysics.phy-astr.gsu.edu/hbase/electronic/opampcon.html#c1>





# Op-Amps for Math

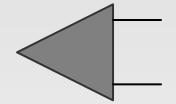

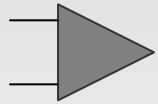
- 
- 
- Inverting
  - Non-Inverting
  - Summing
  - Differencing
  - Integrating
  - Differentiating





# Inverting

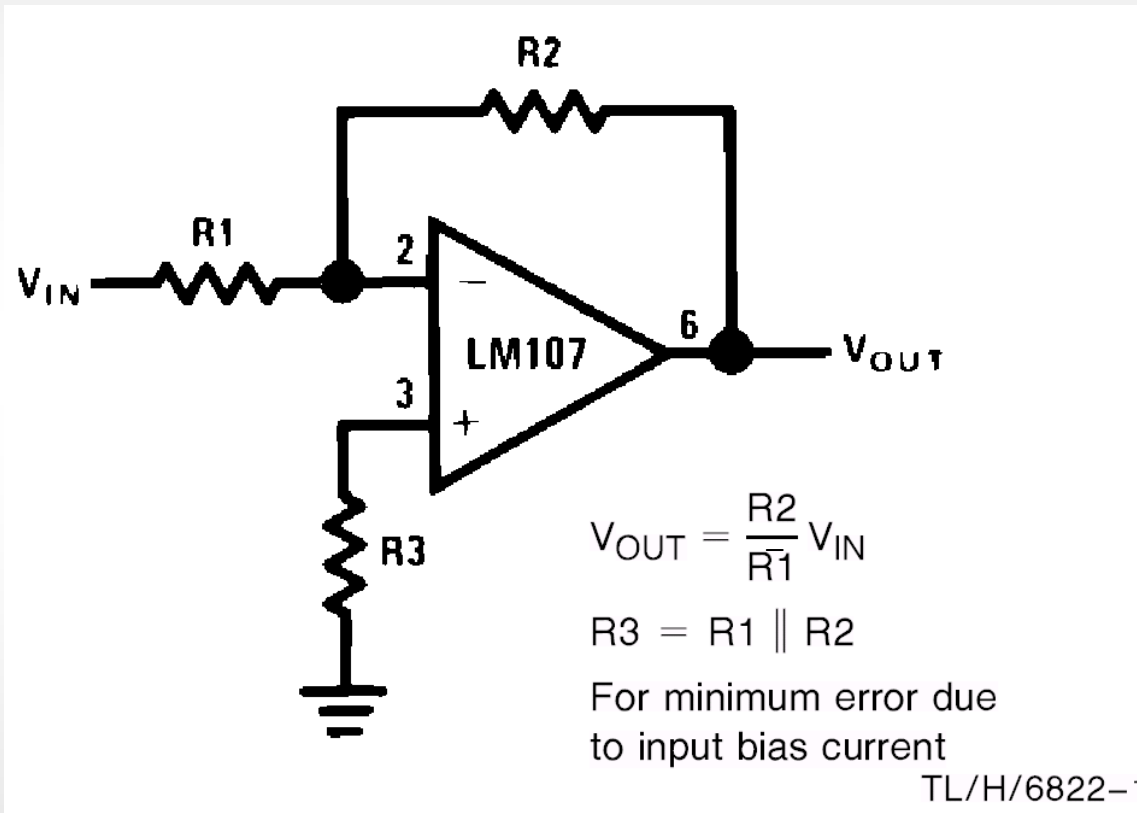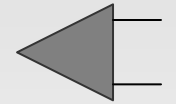

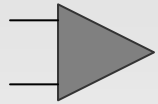"An Application Guide for Op-Amps", National Semi-Conductor, Application Note 20, February 1969.




# Non - Inverting

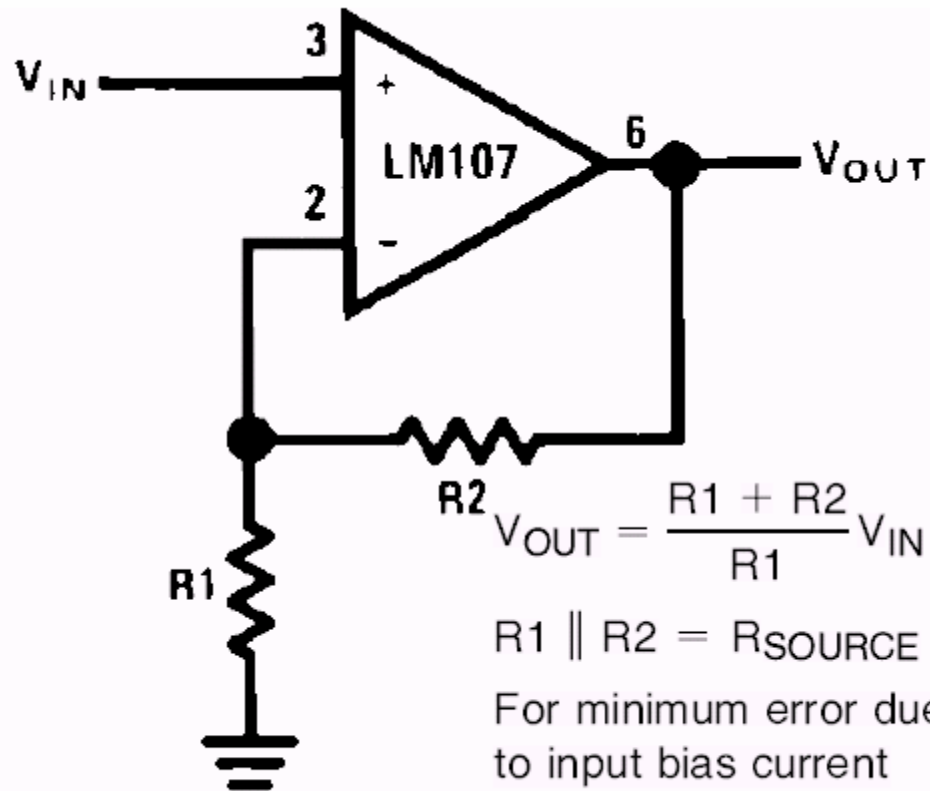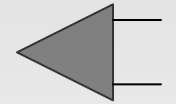

TL/H/6822-2

"An Application Guide for Op-Amps", National Semi-Conductor, Application Note 20, February 1969.

# Summing Op-Amp

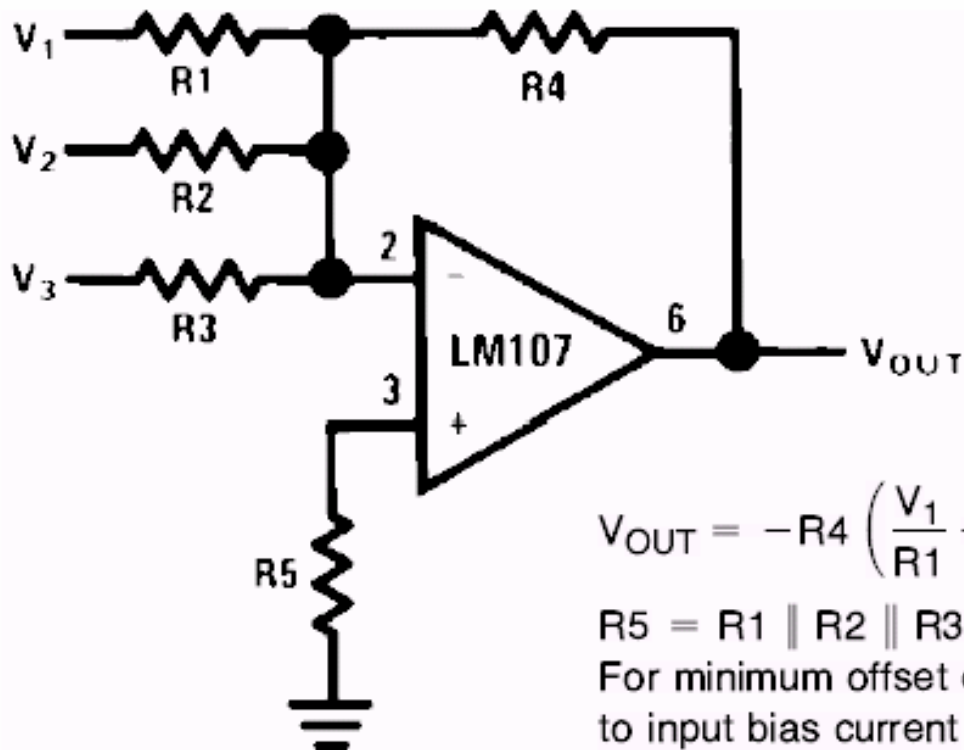


$$V_{OUT} = -R_4 \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

$$R_5 = R_1 \parallel R_2 \parallel R_3 \parallel R_4$$



For minimum offset error due to input bias current

TL/H/6822-4

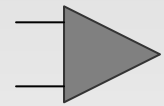
"An Application Guide for Op-Amps", National Semi-Conductor, Application Note 20, February 1969.





# Differencing Op-Amp

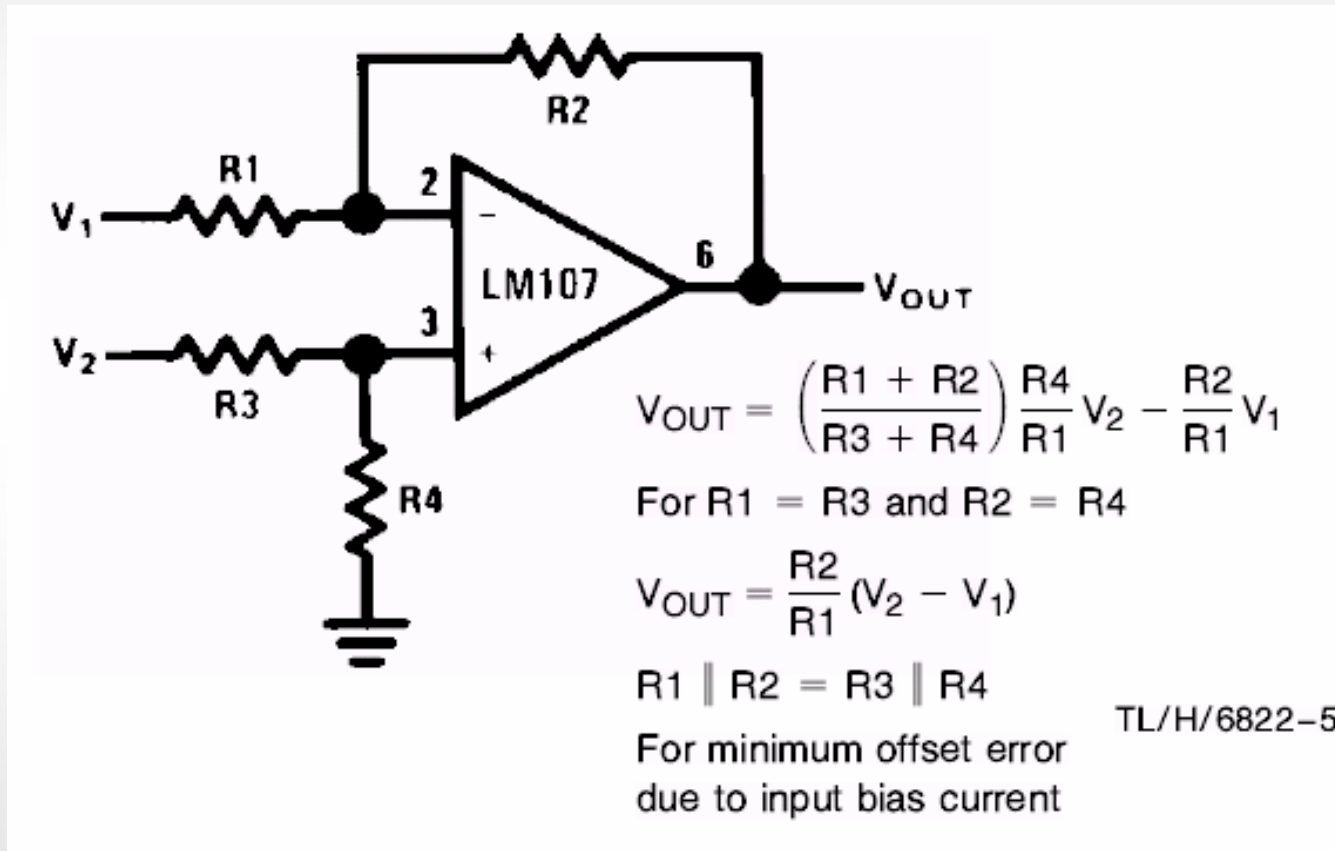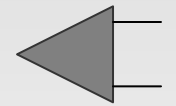

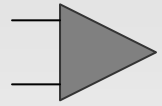"An Application Guide for Op-Amps", National Semi-Conductor, Application Note 20, February 1969.




# Integrating Op-Amp

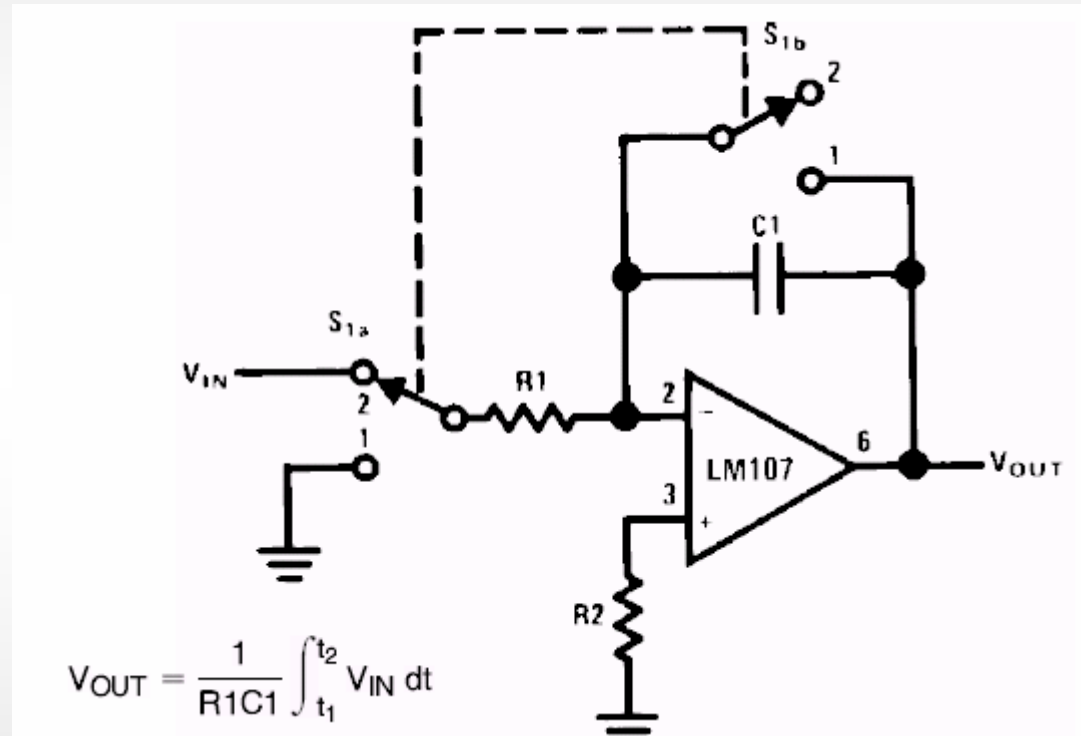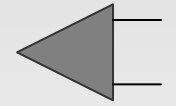


"An Application Guide for Op-Amps", National Semi-Conductor, Application Note 20, February 1969.




# ▶ Differentiating Op-Amp ◀

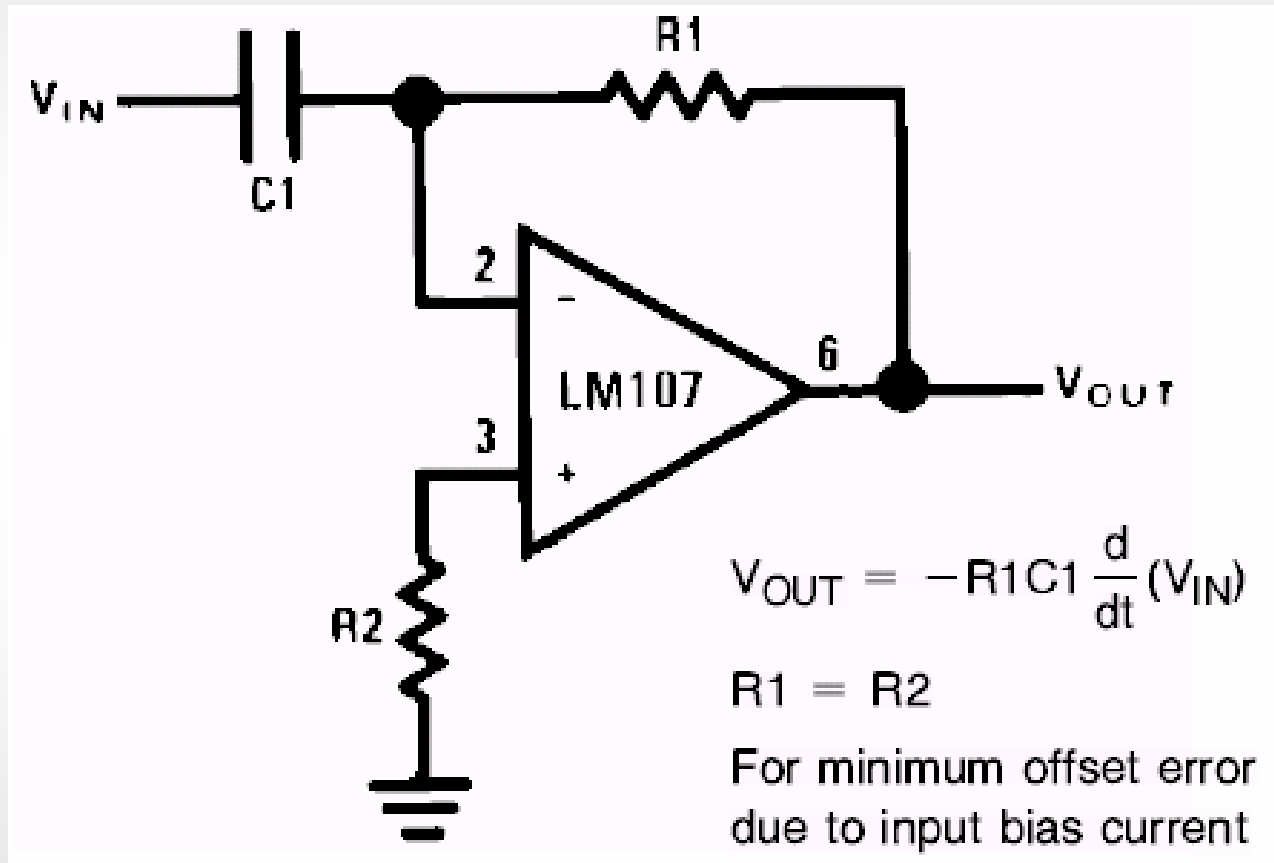

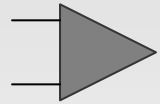"An Application Guide for Op-Amps", National Semi-Conductor, Application Note 20, February 1969.



# Use of an Op amp

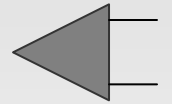

- **Filters:**

**3 types**

**1. Low Pass Filter (LPF)**


- Used to filter higher freq.

**2. High Pass Filter (HPF)**


- used to filter low freq.

**3. Band Pass Filter (BPF)**


- a combination of LPF and HPF

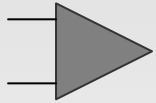


# Contd.

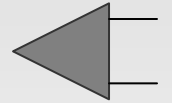

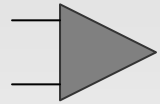- 
- 
- Dual input (dual source - and + with respect to ground),
    - Used in audio equip. control circuits, medical equipment, etc.
  - Single input




# Order of filters

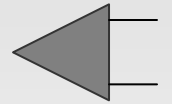



- First order
- Second order

Our examples show second order  
Filters.

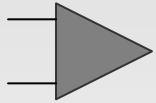- What was the order of the  
filter we used in lab?



# LPF

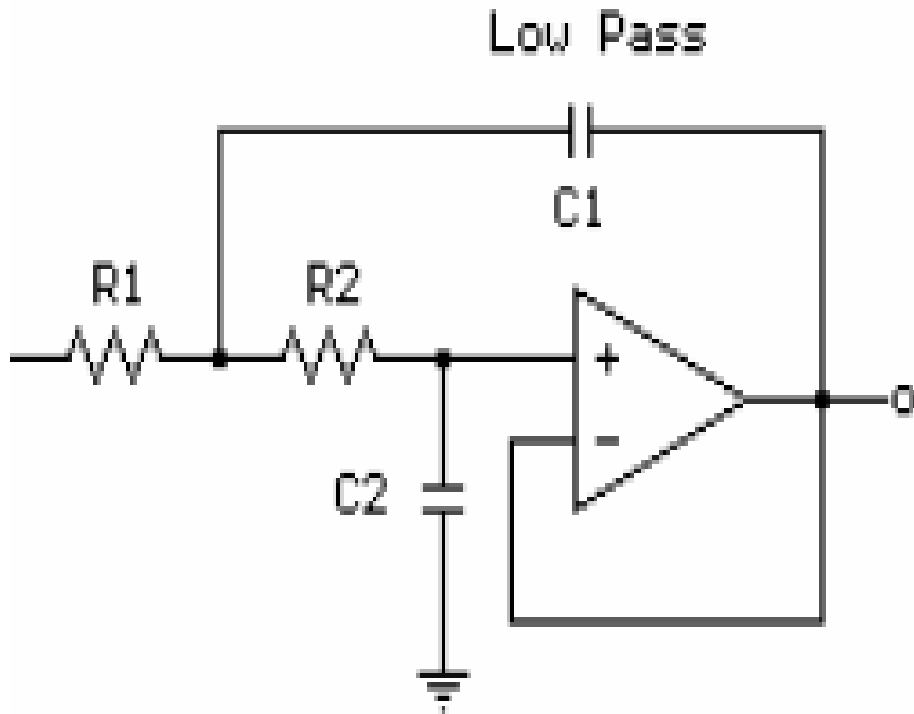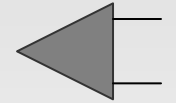

This filter is used to remove noise signals that are above the specified frequency.


The frequency range is given by the equation below

$$f = \frac{1}{2 \pi RC}$$



Where f=freq.

R=R2


C=C1

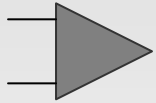



# HPF

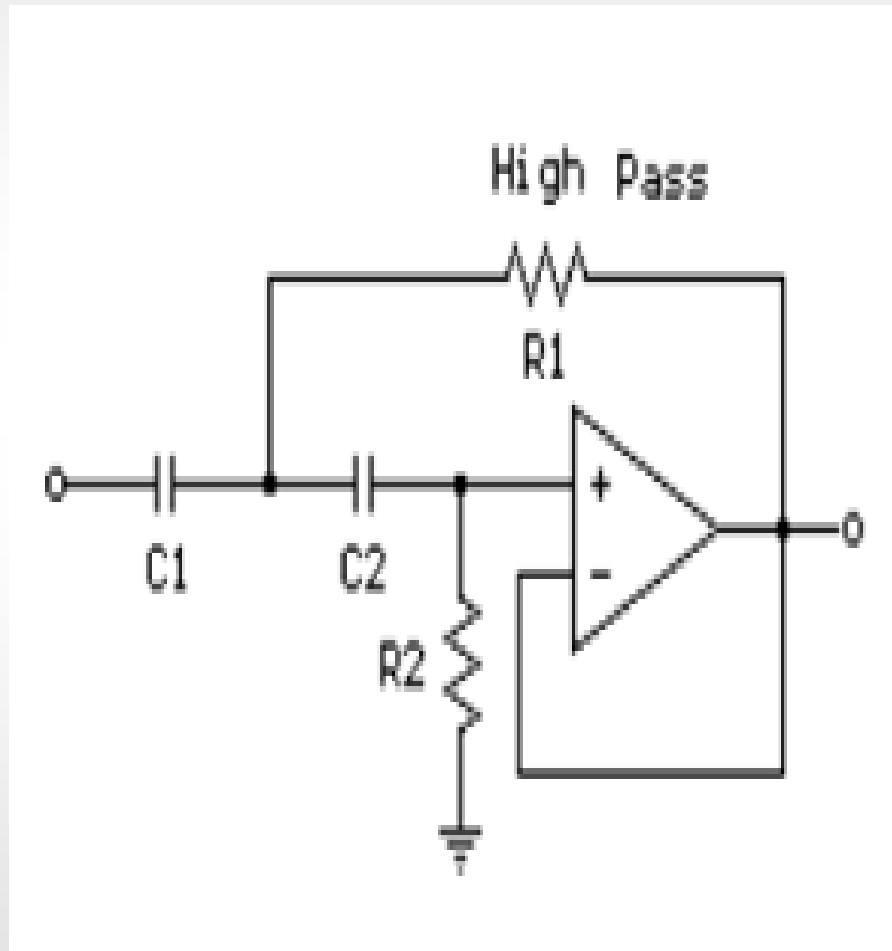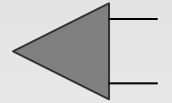

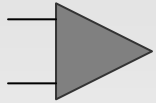
HPF is used to remove all freq. Below the specified freq. and it is Created by reversing the position of the capacitor and resistor In a LPF





# BPF

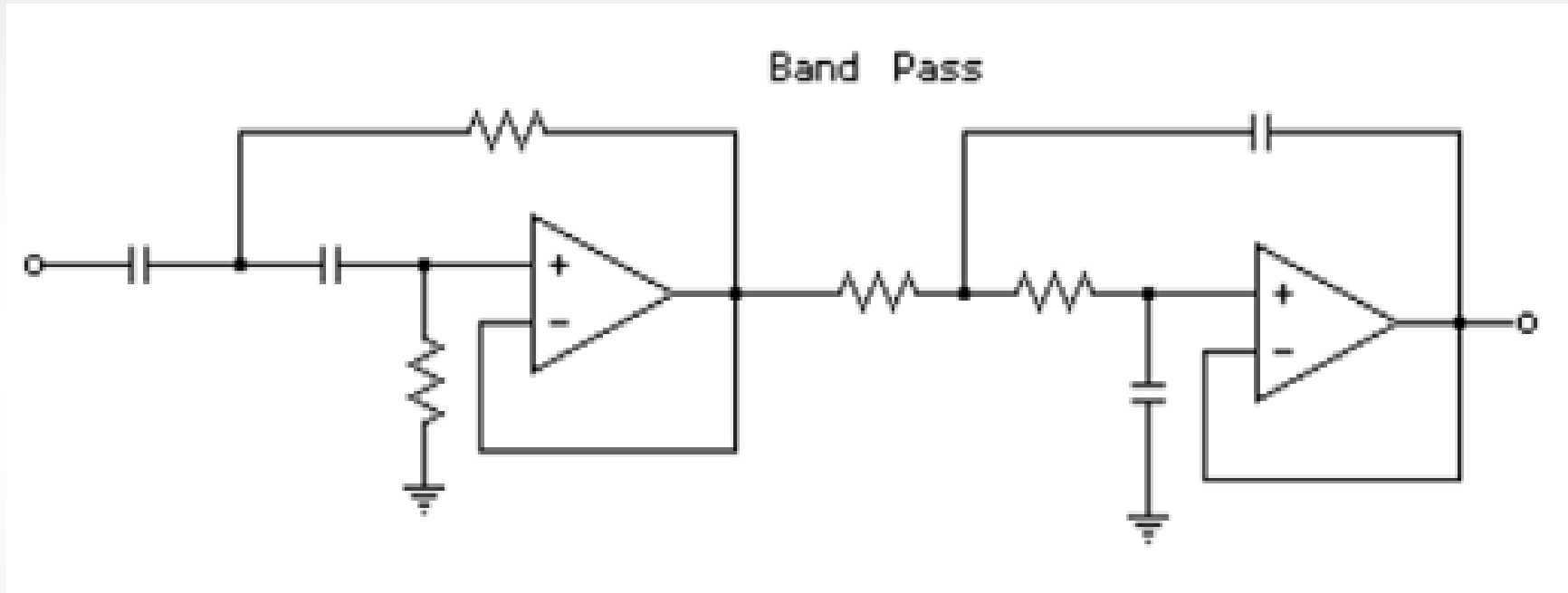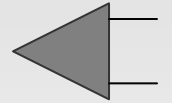

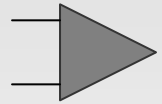This is a combination of the LPF and HPF. It allows for freq. within the range for the LPF and HPF.




# Instrumentation OP Amp

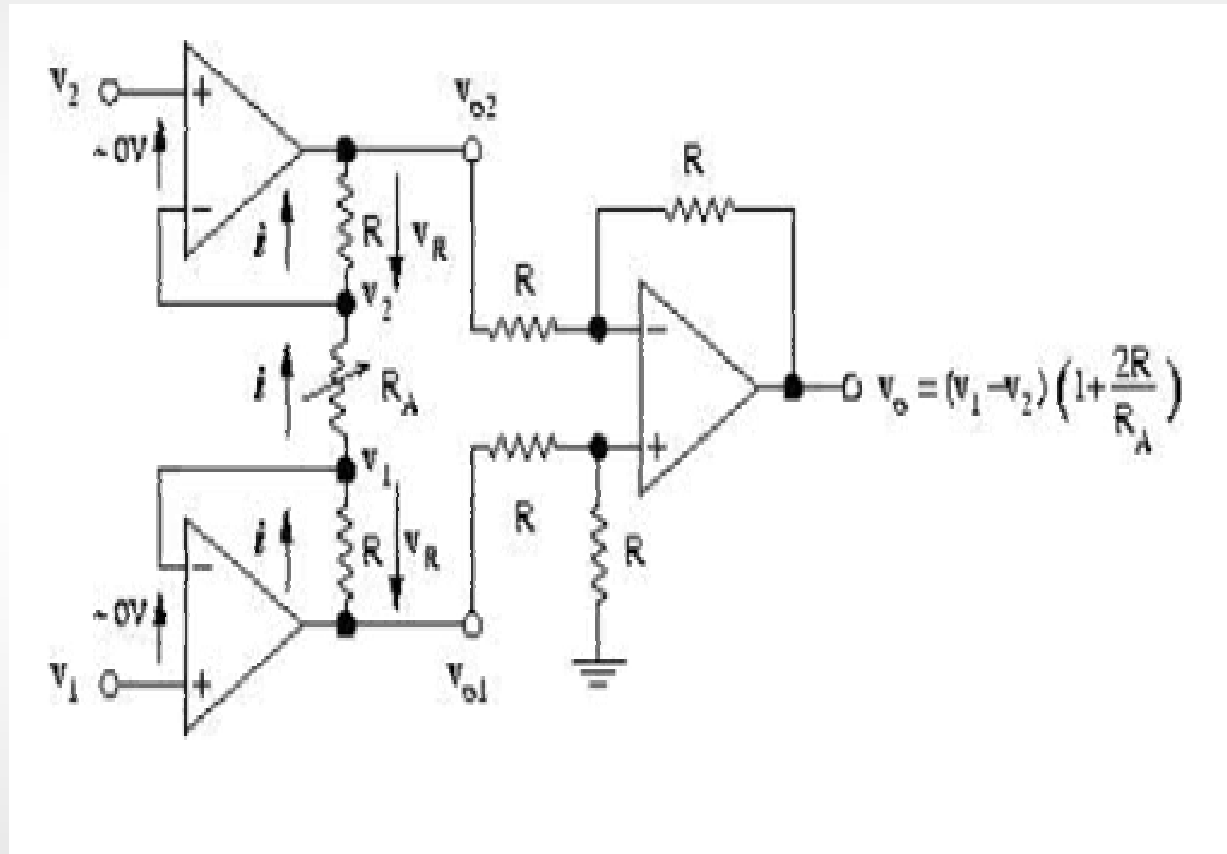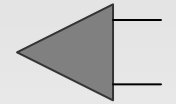


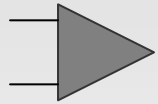This is used in Situations where output voltage needs to varied.







## Analysis of instrumentation op amp

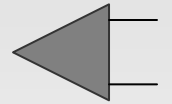

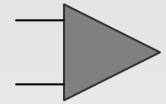
- $V_o = V_{o1} - V_{o2}$
- $V_{o1} = V_1 + V_R$
- $V_{o2} = V_2 - V_R$
- $V_R = (V_1 - V_2) R / R_A$
- $V_o = V_1 - V_2 + 2V_R = (V_1 - V_2) (1 + 2R / R_A)$




# The use of filters

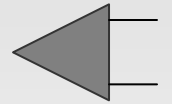

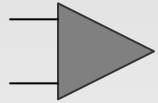
- 
- 
- Communications
  - Removing noise from a power input
  - Radio communications
  - Infrared/ LED signals transm.
  - Etc




# Conclusions

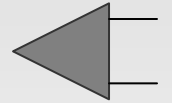

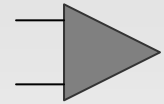- One major disadvantage
  - Distortion when dealing with really low freq. ranges




# Conclusions contd.

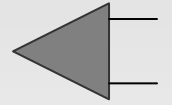


- **Advantages**

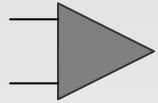- Useable in different industries
- Signal and power amplification
- Simple
- Cheap and easy to build
- Makes life easier
- Math operations



# References

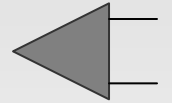

- 
- 
- [www.electronics-tutorials.com](http://www.electronics-tutorials.com)
  - [www.play-hookey.com](http://www.play-hookey.com)
  - Alcitore, Histan Introduction to Mechatronics and Measurement Systems